

ECET 102/CPET 101 Electrical Circuits
Homework 7
Total 80 Points

Assigned Date: Mar. 21, 2012

Due Date: Mar. 28, 2012, before 4:00PM

Hand-In Requirements:

1. Use Microsoft Words to prepare your homework
2. Copy all questions
3. Give detailed calculation to receive full credit
4. Email your hw 7 to both Mr. Sayed Hassan, Lab Instructor at hasssn01@ipfw.edu and Prof. Lin at lin@ipfw.edu

Chapter 7 Series and Parallel Circuits: Problems, pages 276-282, Total 60 points

- Question 5 (10 points)
- Question 9 (10 points)
- Question 12 (15 points)
- Question 23 (10 points)
- Question 27 (15 points)

Chapter 8 Methods of Analysis, pages 332-333, Total 20 points

- Question 1 (10 points)
- Question 7 (10 points)