

ECET 102/CPET 101

Lab 4

MATLAB Exercises Lab

<http://www.etcs.ipfw.edu/~lin>

Feb. 6, 2012

LAB 4 MATLAB Exercise Lab- By P. Lin

1

Lab Activities

1. Plotting Ohm's law ($R = 5$ ohms, $E = 0$ to $30V$)
2. Plotting $R1$ (1 ohms), $R2$ (10 ohms, $E = 0$ to $30V$ on the same plot
3. Calculations for a circuit with 3 resistors in series

Feb. 6, 2012

LAB 4 MATLAB Exercise Lab- By P. Lin

2

1. Plotting Ohm's Law

Problem Statement:

- Build a MATLAB simulation circuit for a variable power supply ($E = 0$ to 30V), an ammeter, and a 5 Ohms connected in series. Write a simple MATLAB program to plot E vs. I (Ohm's law)

Feb. 6, 2012

LAB 4 MATLAB Exercise Lab- By P. Lin

3

1. Plotting Ohm's Law

Solution:

- $R = 5\text{ Ohms}$
- $E = 0, 5, 10, 15, 20, 25, 30\text{ Volts}$ (changed from 0v , increment by 5 v , with the highest voltage 30 V)
- Compute current I for each of the adjusted voltage value

Feb. 6, 2012


LAB 4 MATLAB Exercise Lab- By P. Lin

4

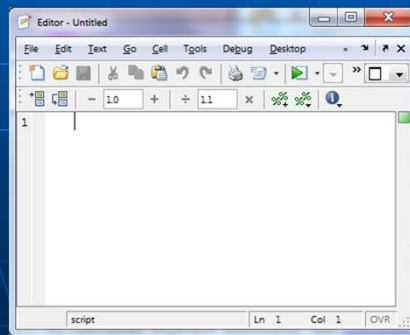1. Plotting Ohm's Law

Step 1: Start=> MATLAB (to see MATLAB application window)

Step 2: Click File => New => Script (to create a M file); and see the Editor as shown below



Feb. 6, 2012

LAB 4 MATLAB Exercise Lab- By P. Lin


5

1. Plotting Ohm's Law

Step 3:

(a). Enter the following 5 statements onto the editor.

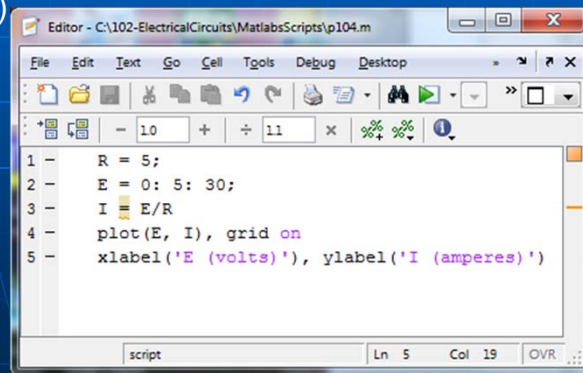(b) File => Save as => P104.m (save it in your own USB flash drive)



Feb. 6, 2012

LAB 4 MATLAB Exercise Lab- By P. Lin

6

1. Plotting Ohm's Law

Step 3:

(C) Debug => Run p104.m (Click on ADD path command if prompted)

Display on the command windows:

I =

0 1 2 3 4 5 6

Feb. 6, 2012

LAB 4 MATLAB Exercise Lab- By P. Lin

7

1. Plotting Ohm's Law


Step 3:

Display on the command windows:

I =

0 1 2 3 4 5
6

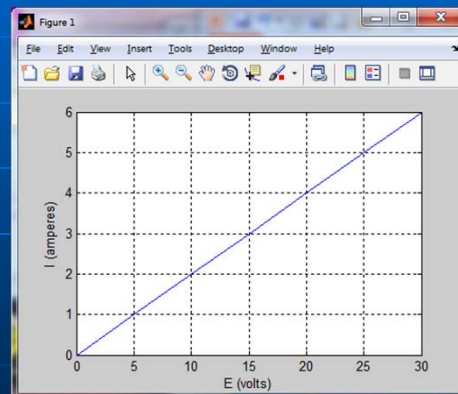And the graphic window
the Ohm's law plot



Feb. 6, 2012

LAB 4 MATLAB Exercise Lab- By P. Lin

8

2. Plotting Two Resistors

Solution:

- $R1 = 1$ Ohms, $R2 = 10$ Ohms
- $E = 0, 5, 10, 15, 20, 25, 30$ Volts (changed from 0v, increment by 5 v, with the highest voltage 30 V)
- Compute currents $I1$, and $I2$ for each of the adjusted voltage value

Feb. 6, 2012

LAB 4 MATLAB Exercise Lab- By P. Lin

9

2. Plotting Two Resistors

MATLAB Solution:

- File => New => Script (create a new script file)
- Enter the following statements, then save it as p105.m

```
R1 = 1;  
R2 = 10  
E = 0: 5: 30;  
I1 = E/R1;  
I2 = E/R2  
plot(E, I1, E, I2), grid on;  
axis([0 30 0 7]);  
xlabel('E (volts)'), ylabel('I (amperes)');  
title('I-V plot for R1 and R2')  
text(6,5,'R1 =1 ohm'), text(20, 3,'R2 =10 ohms');
```


Feb. 6, 2012

LAB 4 MATLAB Exercise Lab- By P. Lin

10

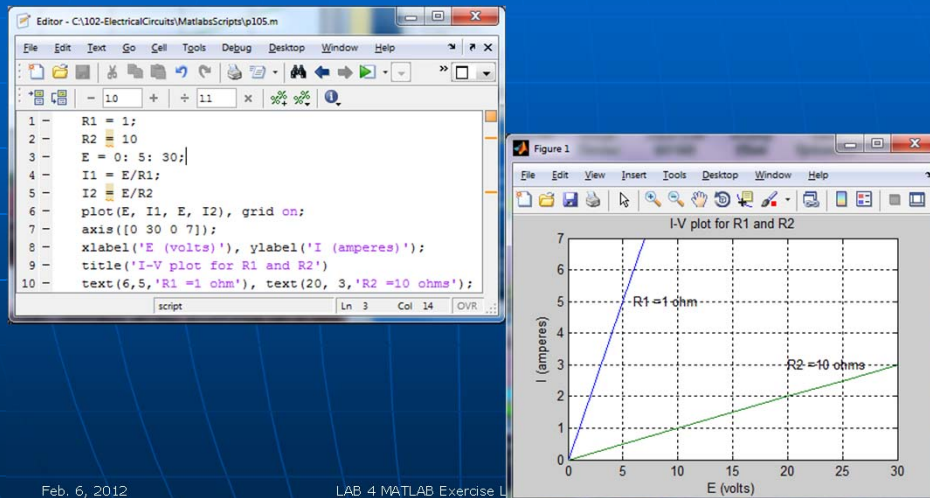2. Plotting Two Resistors

- Debug => Run to execute the script, and its plot



Feb. 6, 2012

LAB 4 MATLAB Exercise L

3. Three Resistor in Series

- Example 3:
Calculating Series Resistance, Current in the circuit, voltage drops across each resistors $R1 = 10\text{ohms}$, $R2=20\text{ohms}$, and $R3 =40\text{ohms}$; and power supply voltage is $E = 10\text{V}$.
- Problem Statement:
 - You are asked by your supervisor to design a MATLAB program for your colleague. This program should allow the user to calculate the total series resistance of a circuit.

Feb. 6, 2012

LAB 4 MATLAB Exercise Lab- By P. Lin

12

3. Three Resistor in Series (continue)

■ Problem Solving Process and Steps:

- Define the problem
- Formulate a mathematical model
- Develop an algorithm
- Write the code for the problem
- Test program and verify the solution
- Document the program and solution

Feb. 6, 2012

LAB 4 MATLAB Exercise Lab- By P. Lin

13

3. Three Resistor in Series (continue)

■ Problem Solving Process and Steps:

1. Define the problem
2. Formulate a mathematical model - Total $R = R_1 + R_2 + R_3 + \dots + R_n$
3. Develop an algorithm
 - Step 3.1: User input $R_1, R_2, R_3, \dots, R_n$, one at a time
 - Step 3.2: Compute subtotal resistance
 - Step 3.3: Repeat until the end of resistance entering
 - Step 3.4: Print total resistance
 - Step 3.5: Calculate total circuit current
 - Step 3.6: Calculate voltage drops V_1, V_2, V_3
4. Write the code for the problem

Feb. 6, 2012

LAB 4 MATLAB Exercise Lab- By P. Lin

14

3. Three Resistor in Series – Solution

■ MATLAB Solution 1

- Understand who users are
 - How to input resistance values?
 - The mathematical model or equation
- Total R = R1 + R2 + R3 + ... + Rn
- How to display or print total resistance value?

```
>> E = 10;
>> r1 = 10; r2 = 20;
>> r3 = 40;
>> r_total = r1 + r2 + r3
r_total =
    70
>> I = E/r_total;
>> V1 = I*r1; V2 = I*r2;
>> V3 = I*r3;
>> E - (V1 + V2 + V3)
E = 0
```

Feb. 6, 2012

LAB 4 MATLAB Exercise Lab- By P. Lin

15

Summary

Feb. 6, 2012

LAB 4 MATLAB Exercise Lab- By P. Lin

16