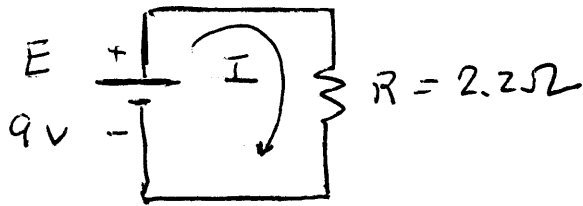


2012/2/1

①

Ex 4.1




OHM'S LAW

$$I = \frac{E}{R} = \frac{9V}{2.2\Omega}$$

$$I = \frac{9}{2.2} = 4.1 \text{ Amp} = 4.09 \text{ Amp OK}$$


$$\begin{array}{r} 4.0909... \\ 2.2 \overline{) 9.0} \\ \underline{8.8} \\ 200 \\ \underline{198} \\ 200 \\ \underline{198} \\ 20 \end{array}$$

Ex 4.2

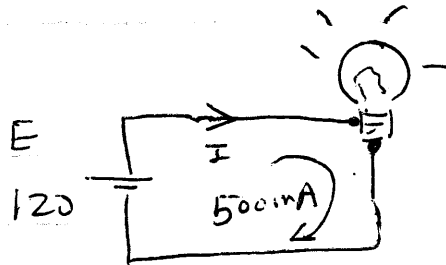

MAP

Ex 4.3

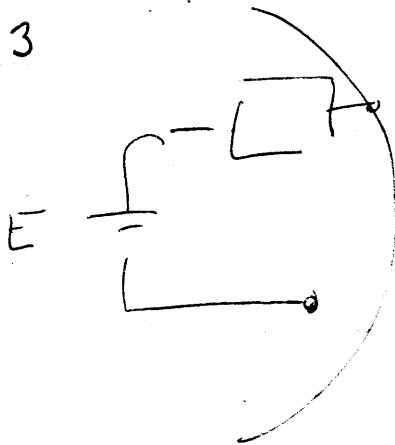

$$I = \frac{E}{R}$$



$$I = \frac{16V}{2k\Omega} = \frac{16V}{2 \times 10^3 \Omega} \text{ Amp}$$

$$\begin{array}{ccc} 3 & -3 & 3-3 & 0 \\ 10 \times 10 & = & 10 & = 10 \\ & & & = 1 \end{array}$$

$$\begin{aligned} &= \frac{16 \times 10^{-3}}{2 \times 10^3 \times 10^{-3}} = 0.008 \text{ Amp} \\ &= \frac{16 \times 10^{-3}}{2 \times 1} = \frac{16}{2} \times 10^{-3} = 8 \text{ mA} \end{aligned}$$

2

Ex 4-4.

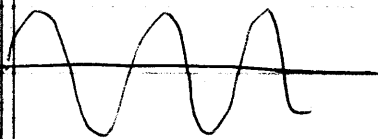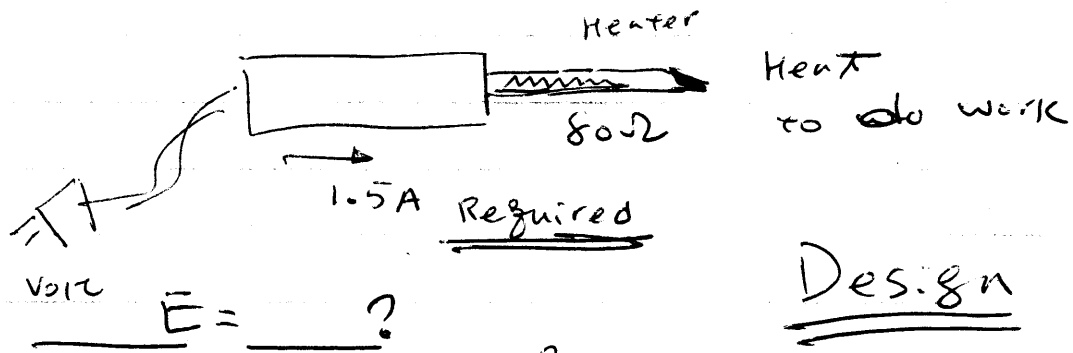

$$I_v = \frac{E}{R_v}$$

Right ~~Left~~ (Known Quantities)

DCV

~~$$I = \frac{E}{R}$$~~

AC

~~$$\frac{I}{1} = \frac{E}{R}$$~~

$$I \cdot R = E \cdot 1 = E$$



$$E = I \cdot R = 1.5A \times 80\Omega = 120 \text{ volts} *$$