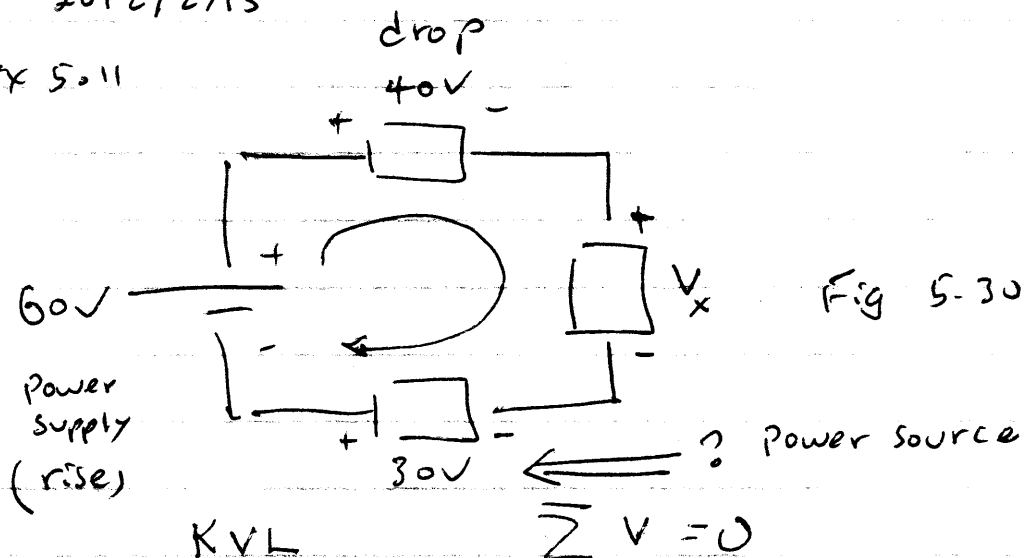


2012/2/15

①

Ex 5.11




rises = Drops

$$60V + 30V = 40V + V_x$$

$$90V = 40V + V_x$$


$$V_x = 90 - 40 = \underline{50V} \Rightarrow$$

Ex. 5.12

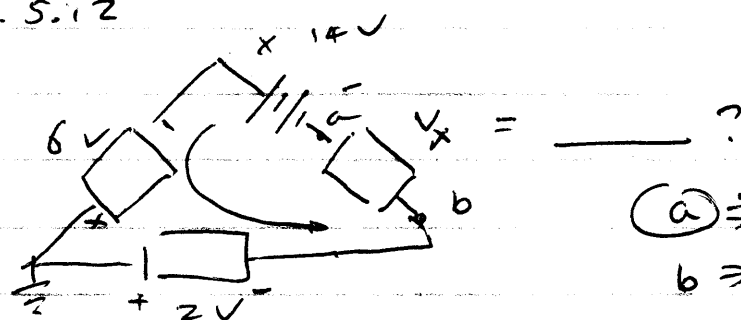

(a) $\Rightarrow - +$

b $\Rightarrow - +$ Blind?

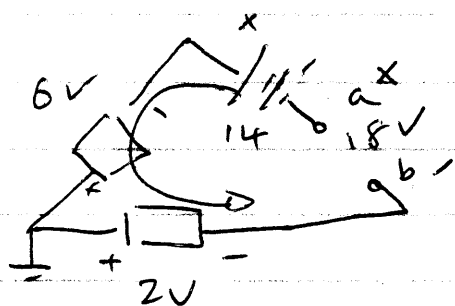

$V_{ab} = ?$

$$14V + 6V - 2V + V_{ab} = 0$$

$$\begin{array}{ccc} 14V & + & 6V \\ \text{rise} & & \text{rise} \end{array} = \begin{array}{c} 2V \\ \text{drop} \end{array} + V_{ab}$$

$$20V = 2V + V_{ab}$$

$$V_{ab} = 18V$$

$$14 + 6 - 2 + V_{ba} = 0$$


$$18 + V_{ba} = 0$$

$$V_{ba} = -18V$$

$$\boxed{V_{ab} = 18V} \quad \odot$$

EX. 5.13

(2)

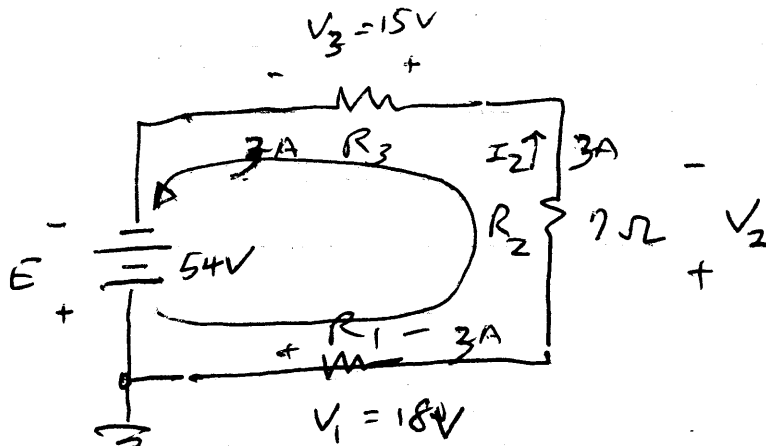

$$E = V_1 + V_2 + V_3$$

$$54 = 18 + V_2 + 15$$

$$V_2 = 54 - (33) = 21 \text{ V}$$

OHM's Law

$$I_2 = \frac{V_2}{R_2} = \frac{21 \text{ V}}{7 \Omega} = 3 \text{ A}$$

Power Consumption

$$P_T = P_1 + P_2 + P_3 = I^2 R_1 + I^2 R_2 + I^2 R_3 \quad (?)$$

$$= 9(R_1 + R_2 + R_3)$$

$$P_T = P_1 + P_2 + P_3$$

$$= V_1 \cdot I + I^2 R_2 + V_3 \cdot I$$

$$= (3 \times 18) + (9 \times 7) + (3 \times 15)$$

$$= 54 \text{ W} + 63 \text{ W} + 45 \text{ W} = 162 \text{ Watts}$$

Running for
2 hr

$$\text{KWH} = 162 \text{ W} \times 2 \text{ hr} = 324 \text{ WH}$$




$$= 0.324 \text{ KWH}$$

$$\begin{array}{r} 63 \\ 54 \\ 45 \\ \hline 162 \end{array}$$


(3)

5V

V_{CC}

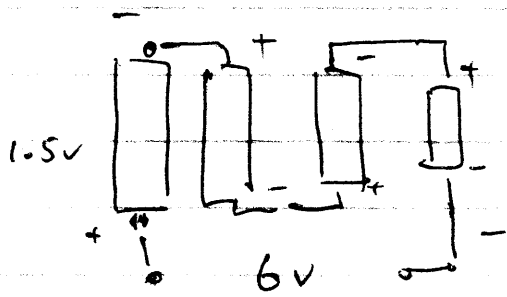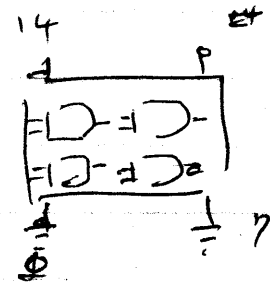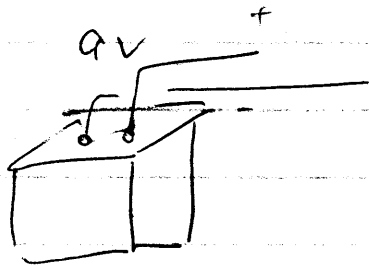

Zener
5.1V

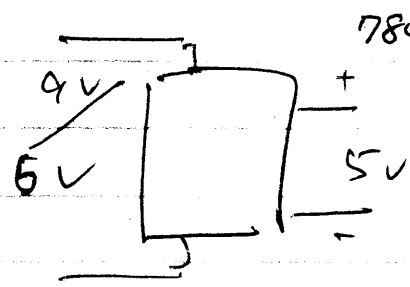

7805 5V IC regulator