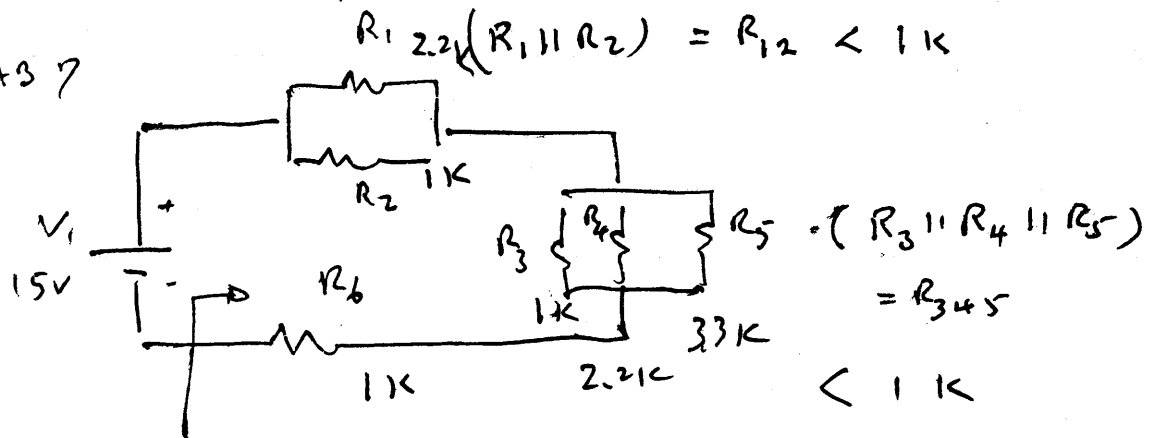



2012/2/27

①


LAB 7




Mouser / Digkey

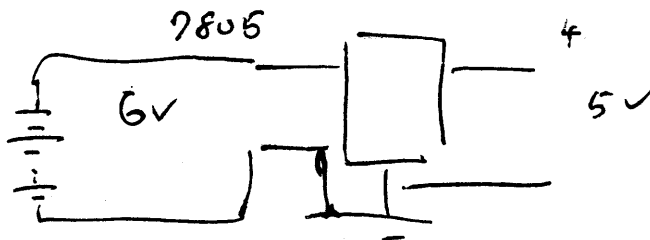

7812

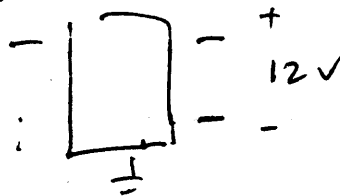
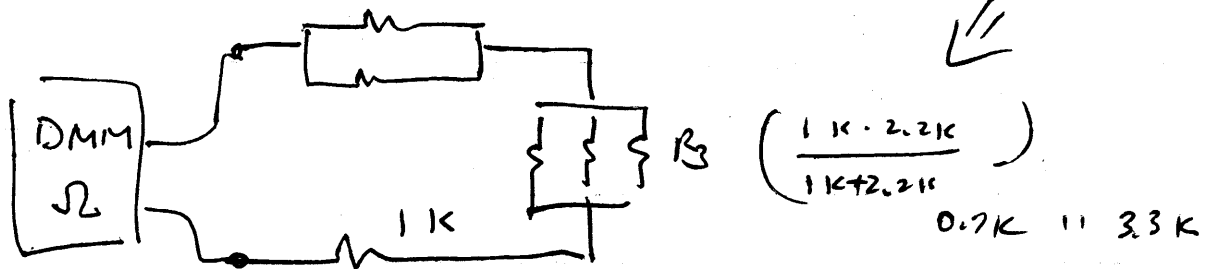
$$0.75k = \frac{2.2 \times 1.1k}{2.2 + 1.1k} = \frac{2.2}{3.2} k$$




$$R_T = R_{12} + R_{345} + R_6 \approx 3k$$

$$\begin{aligned}
 & \frac{0.7 \times 3.3}{0.7 + 3.3} \\
 &= \frac{2k}{4k} \\
 &\approx 0.5k
 \end{aligned}$$

Current Divider Rule

(2)

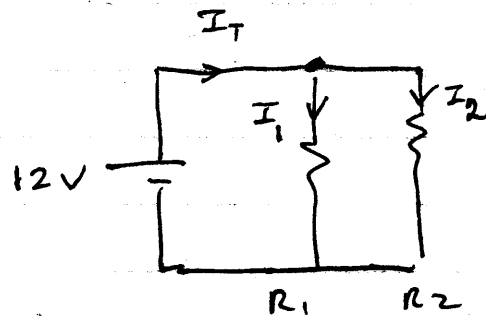

$$= \frac{12V}{R_1} = \frac{12V}{R_2}$$

$I_1 \quad I_2$

1 K 1 K


12 mA 12 mA

1 K 2 K

12 mA 6 mA

Given I_T Find $I_1 = I \cdot \frac{R_2}{R_1 + R_2}$

$$I_2 = I \cdot \frac{R_1}{R_1 + R_2}$$

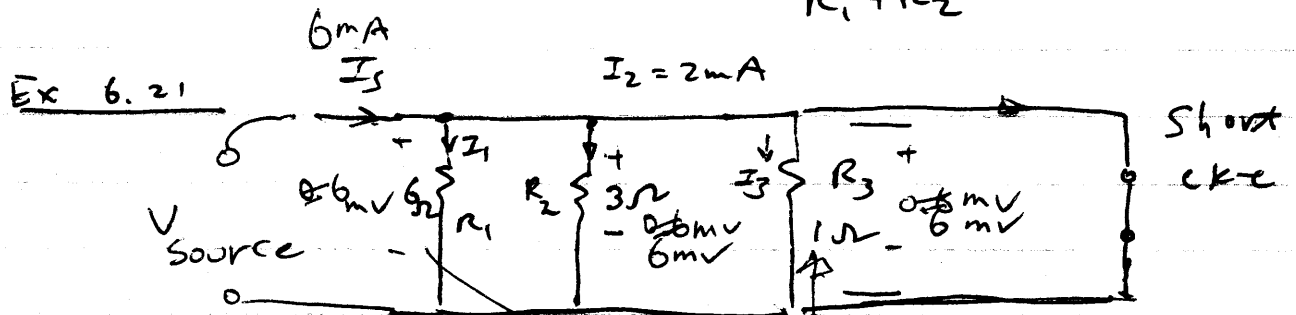

Step 1) Find $V_{R2} = I_2 \cdot R_2 = 2mA \cdot 3\Omega = 6mV$

Step 2) Apply $V_{R2} = V_{R3} = V_{R1}$

Step 3) Compute $I_1 = \frac{V_{R1}}{R_1} = \frac{6mV}{6\Omega} = 1mA$

Compute $I_3 = \frac{V_{R3}}{R_3} = \frac{6mV}{1\Omega} = 6mA$

Step 4) $I_S = I_1 + I_2 + I_3$

$$= 1mA + 2mA + 6mA$$

$$= 9mA$$

$$V_{Source} = V_{R1} = V_{R2} = V_{R3} = 6mV$$


(3)

N Resistors

$$I_x = \frac{(R_T \cdot I_T)}{R_x} \leftarrow \text{Ohm's Law} = \frac{E}{R_x}$$

COR for two resistors in parallel
 I_T
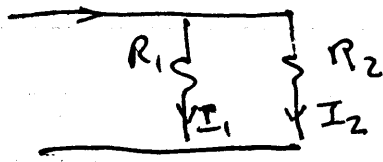
$$R_T = \frac{R_1 \cdot R_2}{R_1 + R_2}$$




Find

$$I_1 = \frac{R_T \cdot I_T}{R_1} = \left(\frac{\left(\frac{R_1 \cdot R_2}{R_1 + R_2} \right) \cancel{R_1}}{\cancel{R_1} / R_1} \right) \cdot I_T$$


$$= \left(\frac{\frac{1 \cdot R_2}{R_1 + R_2}}{1} \right) I_T = \left(\frac{R_2}{R_1 + R_2} \right) \cdot I_T$$

$$I_2 = \left(\frac{R_1}{R_1 + R_2} \right) I_T$$


④

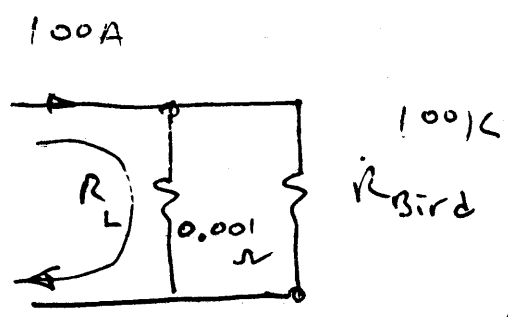

$R_{Bird} \approx 100k\Omega$


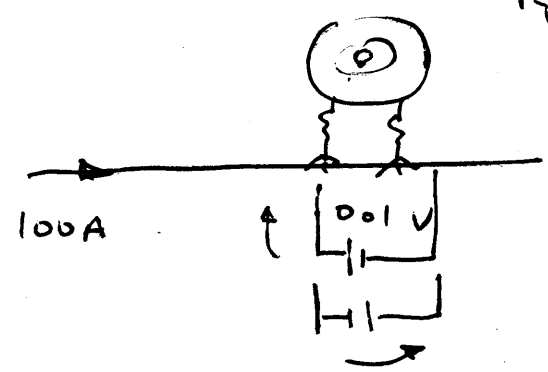


Flux

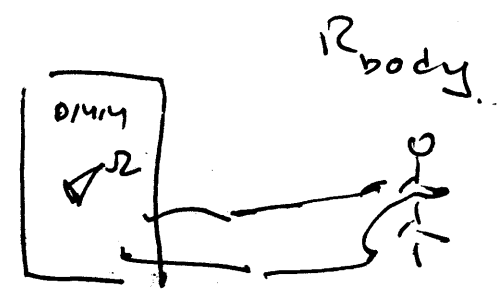

$$V_{R_L} = 100A \cdot R_L = 0.1V$$

3.8V
9V

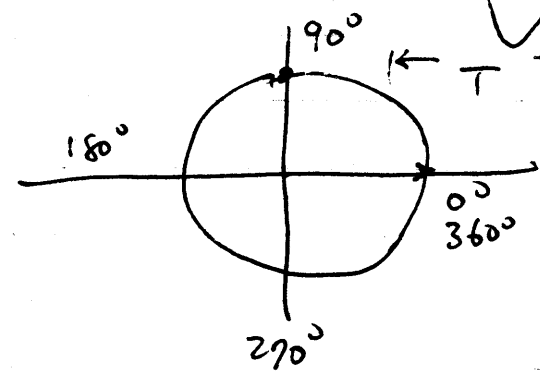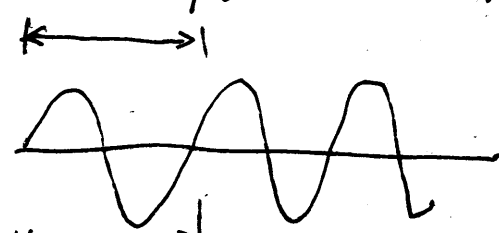

Trig.

$f = 60Hz$


$$T = \frac{1}{f} = \frac{1}{60} = 16.67ms$$

$\rightarrow 8.87msec \Rightarrow 0.0089sec$


$\leftarrow 8.87msec$

5

DMM MA Meter

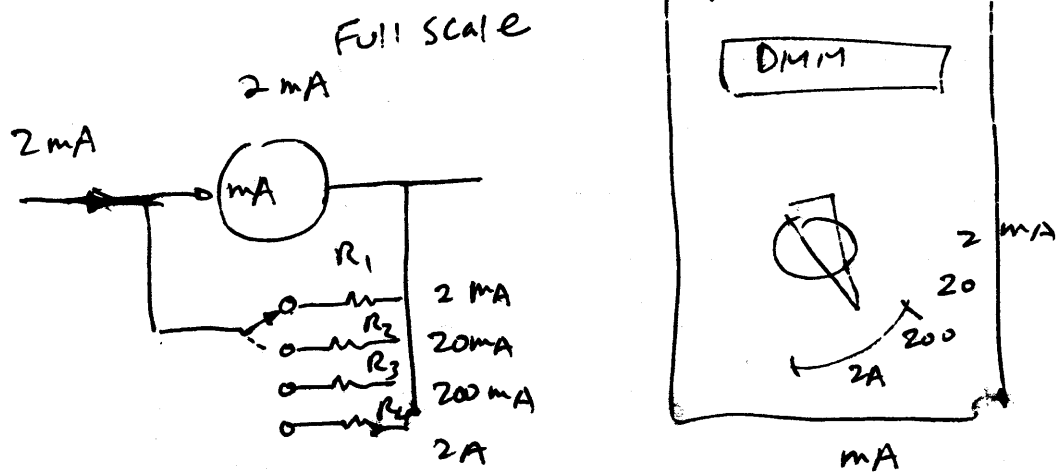

R_1 R_2 R_3 R_4

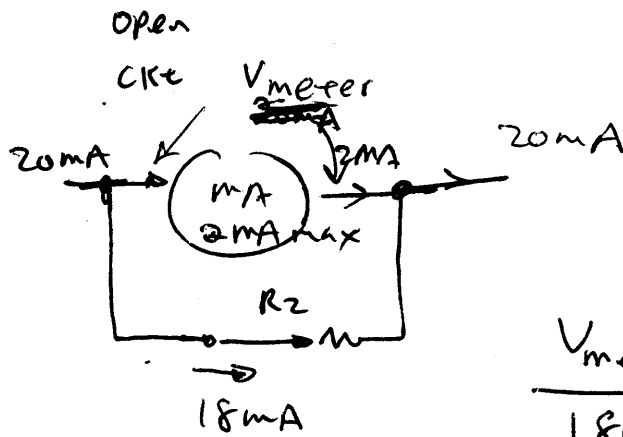


$$\frac{V_{meter}}{18mA} = R_2 \quad \text{design}$$

Shunt

shunt resistor.

$$R_2 \ll (MA) \text{ Resistance}$$

Voltage Sources in parallel

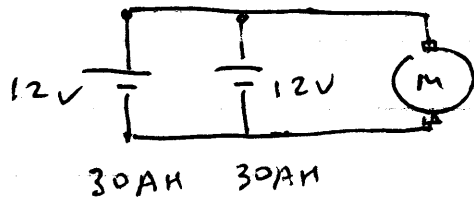


DC motor / Electric Bike

Use one BA - 20 miles


Use both BA₁ + BA₂

→ > 30 miles

? 40 miles ?

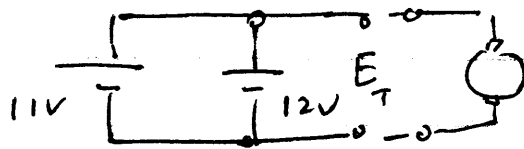


$$E_T = 11V$$

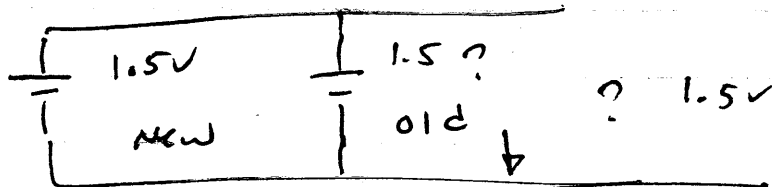

42V Solar cell 15W

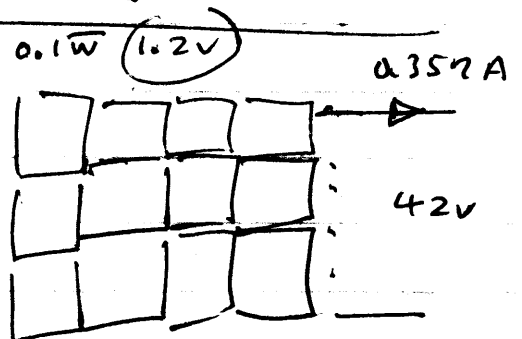- Each cell output 0.1W / 1.2V
- How many in parallel/series would be needed.



$$P = E \cdot I \quad 15W = 42 \cdot I$$

$$I = 0.357A$$


$$\text{Each cell} \quad 0.1W = E \cdot I = 1.2 \cdot I$$

$$I = \frac{0.1W}{1.2} = 0.083A$$

$$I_x = \frac{I}{N_{\text{parallel}}} = 0.083A = \frac{0.357A}{N_p}$$

$$N = \frac{0.357}{0.083} = 4.3 \approx 5$$

67

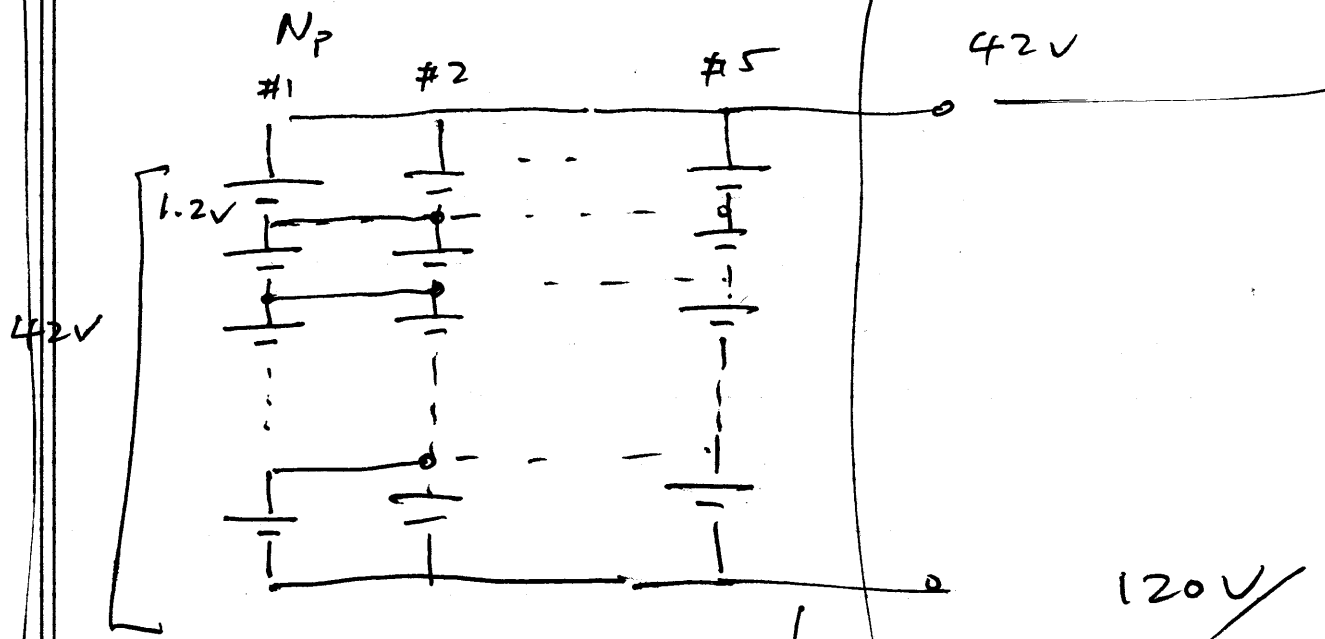

$$N_s = \frac{42V}{1.2V} = 35$$

$$\frac{120V}{45W}$$

120V

