

2012/3/12

①

1. Review of EXAM 2 Coverage — March 14

2. LAB 8 (Theory)


Ch 8-1, 8-2 current source

Current $\leftrightarrow$ voltage source conv.

Ch 9-2. Superposition Theorem



$$\sum F = F_1 + F_2 = 0$$

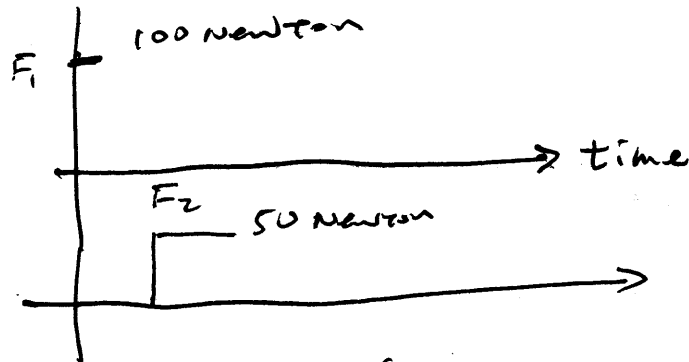

$$F_1 - F_2 = (100 - 50) = 50 \text{ Newtons}$$

Vector : magnitude 50 newton

Direction (Left to Right)


(2)

Multiple Sources

$$10x_1 + 5y_1 = 20$$

$$5x_1 - 10y_1 = 5$$


15V working alone $\Rightarrow V_{A_1}'$

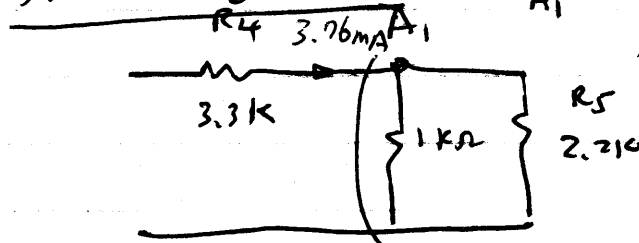

* Determinant method.

* Matrix

$$V_{A_1}' = 2.587 \text{ V}$$

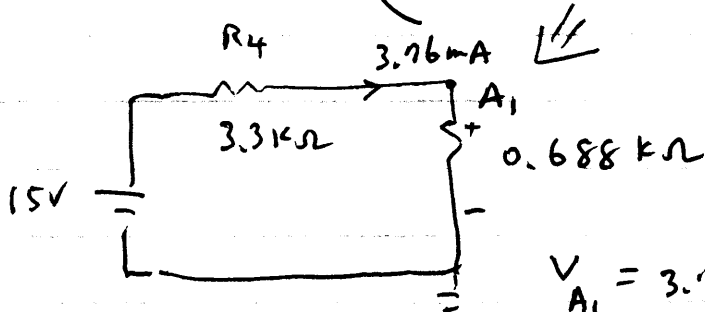

$$V_{A_1} = 3.76 \text{ mA} \times 0.688 \text{ k}\Omega = 2.587 \text{ volt}$$

~~$= 0.14 \text{ volt}$~~


KVL

$$\begin{aligned} 15 \text{ V} &= (3.3 \text{ k} - 3.76 \text{ mA}) + V_{A_1}' \\ &= 12.4 + 2.587 \text{ V} \\ &\approx 15 \text{ V} \end{aligned}$$



5V working alone $\Rightarrow V_{A_1}''$

(3)

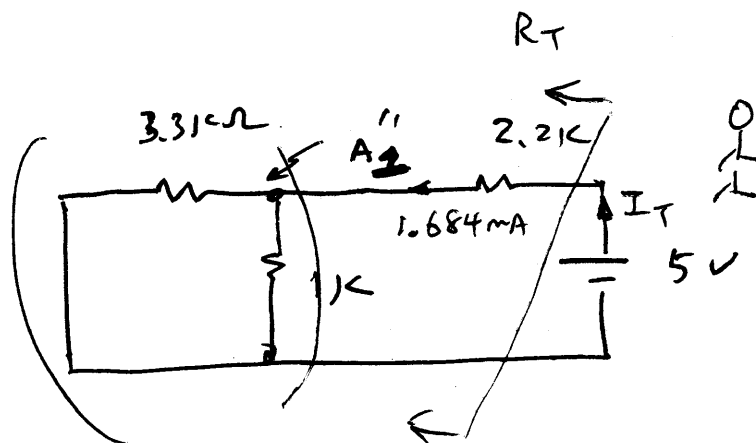

$$\begin{aligned}
 R_T &= 2.2k + (1k \parallel 3.3k) \\
 &= 2.2k + \frac{1k \times 3.3k}{1k + 3.3k} \\
 &= 2.2k + \boxed{0.7674 k\Omega} \\
 &= 2.9674 k\Omega
 \end{aligned}$$

$$I_T = \frac{5V}{R_T} = \frac{5V}{2.9674 k\Omega} \doteq \frac{5V}{2.97 k\Omega} = 1.684 \text{ mA}$$

$$\begin{aligned}
 V_{A1}'' &= I_T \cdot (3.3k \parallel 1k\Omega) \\
 &= 1.684 \text{ mA} \times 0.7674 k\Omega = 1.29 \text{ volt}
 \end{aligned}$$


$$m \times k = 1$$

$$\begin{aligned}
 V_A &= V_{A1}' + V_{A1}'' \\
 &= 2.587V + 1.29V \\
 &= \underline{3.88V} \quad \#
 \end{aligned}$$

Ex 8-1

OHM's Law

Voltage drop across R_1

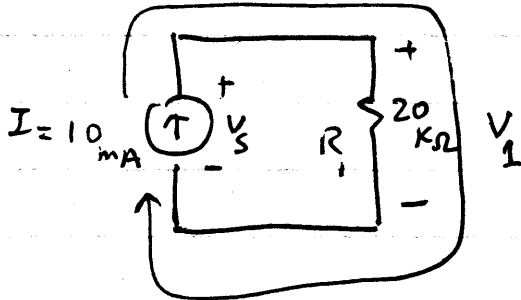


$$V_1 = I \cdot R_1 = 200 \text{ Volt.}$$

$$= 10 \text{ mA} \cdot 20 \text{ k}\Omega$$


$$= 10 \times 10^{-3} \text{ A} \times 20 \times 10^3 \Omega$$

$$10^{-3} \cdot 10^3 = 10^0 = 1$$


KVL $V_S = ?$
 $= V_1 = 200 \text{ V}$

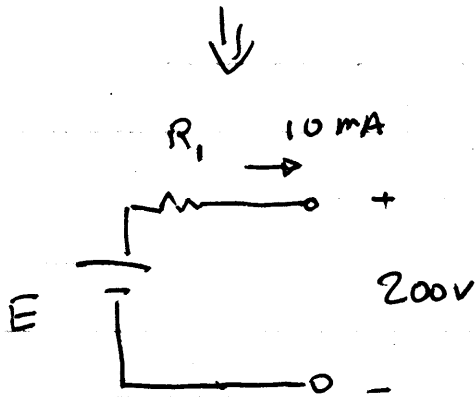

5

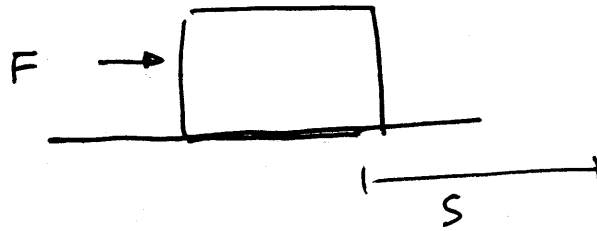


$$W = F \cdot S$$

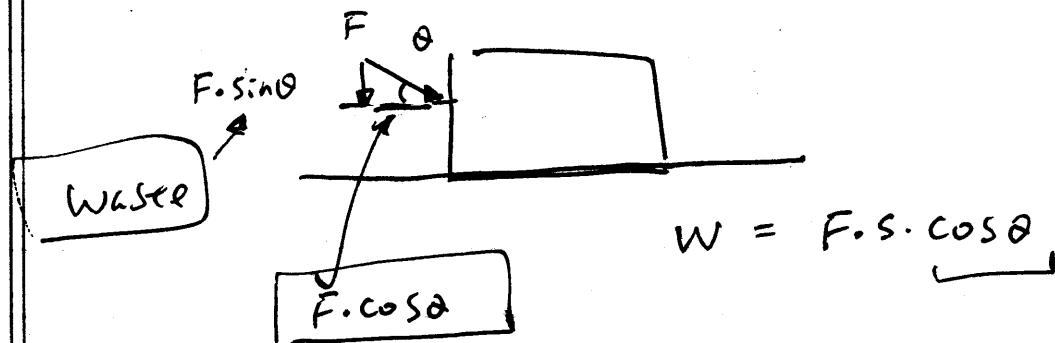

(6)

Ex 6.29

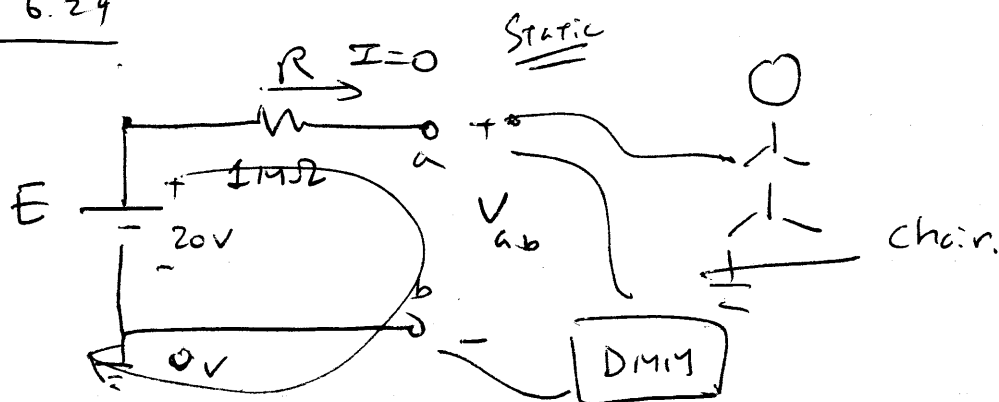

$$V_{ab} = V_a - V_b$$


$$= V_a - 0$$

$$\because I=0 \quad \therefore V_a = E = 20V$$

KVL

$$E = I \cdot R + V_{ab}$$

$$E = V_{ab} = 20V$$

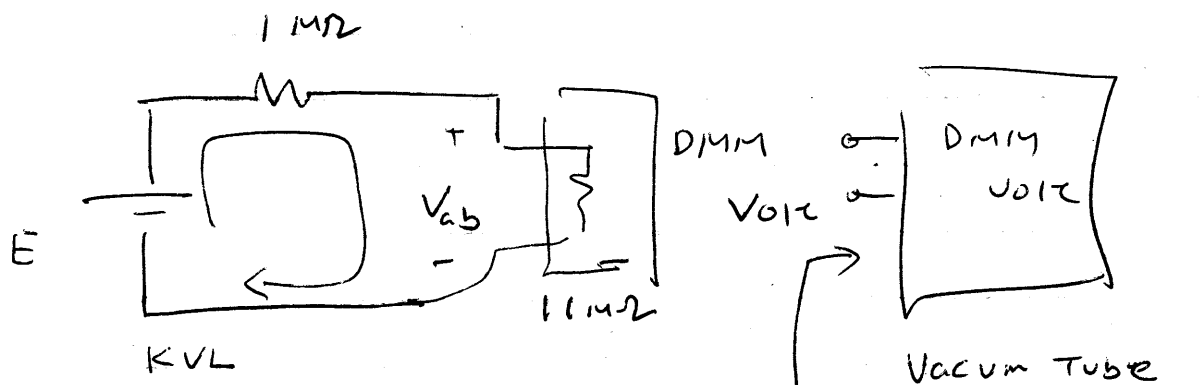

KVL
Voltage Divider Rule

VDR

$$V_{ab} = \left(\frac{11M\Omega}{11M + 1M} \right) E = 20 \cdot \frac{11}{12} = 18.33V$$

KVL

$$E = I \cdot 1M + I \cdot 11M\Omega$$

$$I = \left(\frac{E}{11M\Omega} \right) \Rightarrow 11M\Omega$$