



2012/3/19

①

- 1) Ex 8.9 MATLAB Solution / Branch-Current Analysis
- 2) Ex 8.10 MATLAB Solution
- 3) Ex 8.12 MATLAB / Mesh Analysis

Ch. 7.

Fig 7.2

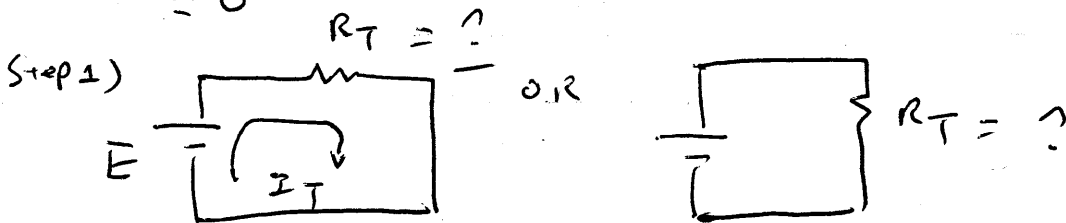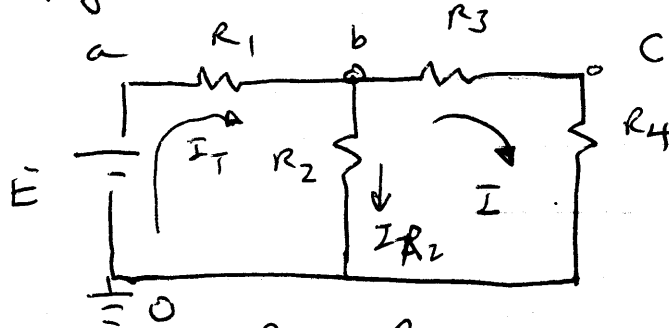

Step 2) $I_T = \frac{E}{R_T}$

Step 3) $I_T \cdot R_1$

Step 4) $V_{bo} = V_b = E - V_{R_1}$

Step 5) $I_{R_2} = \frac{V_b}{R_2}$




Step 6)

$$I = I_T - I_{R_2}$$


...

(2)

Ex 2.1

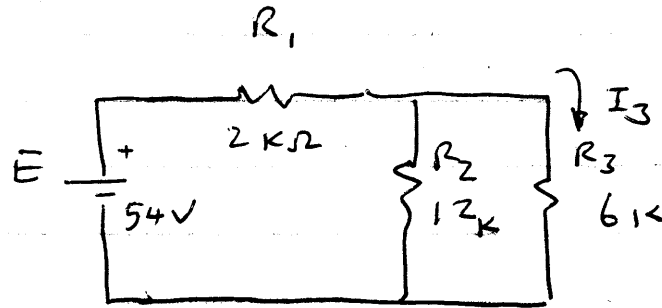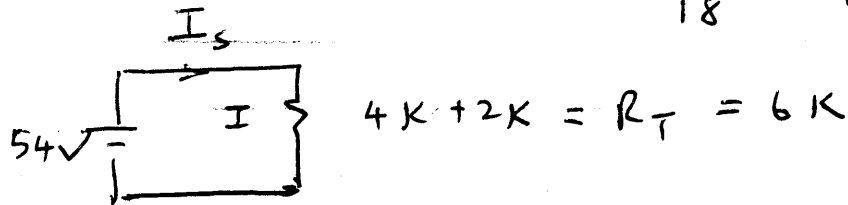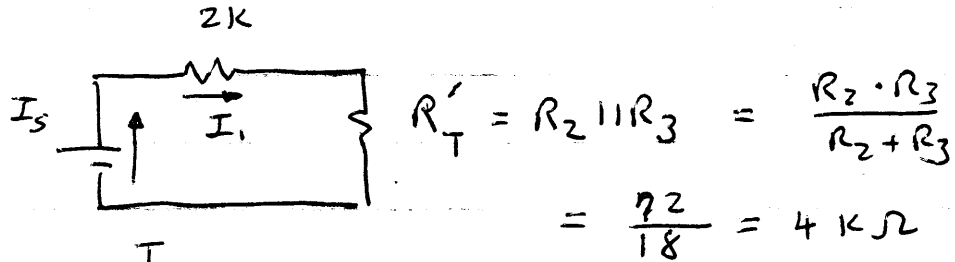
Sol
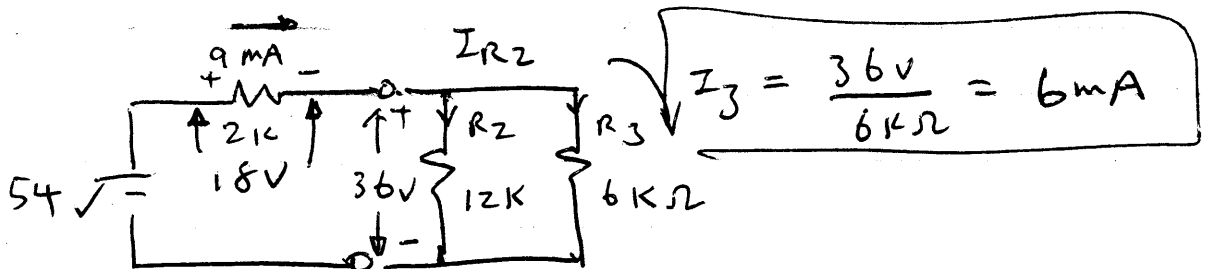
$$I_S = \frac{E}{R_T} = \frac{54 \text{ V}}{6 \text{ k}} = 9 \text{ mA} = I_1$$




$$54 - 18 = 36 \text{ V}$$

$$\frac{36 \text{ V}}{12 \text{ k}} = 3 \text{ mA} = I_{R2}$$

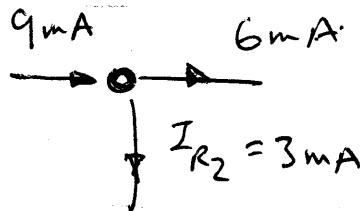KCL

(3)

Ex 7-2.

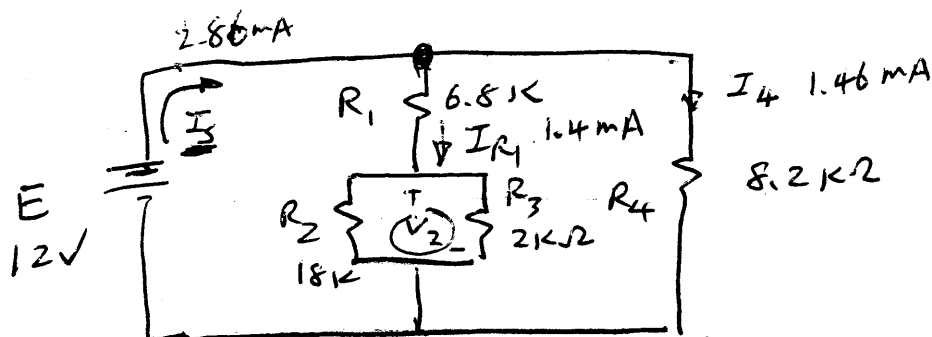

$$R_T = (R_1 + (R_2 \parallel R_3)) \parallel R_4$$

$$R_2 \parallel R_3 = 2k \parallel 18k = \frac{36}{20} = 1.8k\Omega$$

$$R_1 + (R_2 \parallel R_3) = 6.8 + 1.8 = 8.6k\Omega$$



$$R_T = \frac{8.6 * 8.2}{8.6 + 8.2} = 4.2k\Omega$$

$$\boxed{I_S} = \frac{E}{R_T} = \frac{12}{4.2k} = \underline{2.86mA} \quad \#$$

$$\boxed{I_4} = I_S \cdot \frac{8.6k}{8.6k + 8.2k} \quad \text{C D R}$$

$$= \underline{1.46mA} \quad \#$$

$$I_{R_1} = I_S - I_4$$

$$\boxed{V_2} = I_{R_1} \cdot (R_2 \parallel R_3) \leftarrow$$

$$= 1.4mA \cdot 1.8k\Omega = \underline{2.51V}$$