

## ECET 102/CPET101

### Lab 5 Parallel Circuit Lab

By Prof. Paul I. Lin

#### Required Devices & Equipment:

Resistors:  $820\Omega$  x 1,  $1.2k\Omega$  x 2  
Bread board x 1 with wires, wire strippers and cutters  
Variable Power Supply x 1  
Digital Multimeter (DMM) x 1

#### Objectives:

1. Learn parallel resistor circuits and measurement.
2. Learn to use the circuit design and simulation program, Multisim, for circuit analysis.
3. Verify Kirchoff's Current Law (KCL)

#### Procedure:

##### Part 1. Three Resistor in Parallel and Current Measurement

- a) Use a DMM to measure the resistance of the three resistors R1, R2, and R2 and record the values:


$$R1 = R_{820} = \underline{\hspace{2cm}} \Omega$$

$$R2 = R_{1.2k} = \underline{\hspace{2cm}} \Omega$$


$$R3 = R_{1.2k} = \underline{\hspace{2cm}} \Omega$$

- b) Manually calculate the total circuit resistance  $R_t = 1/(1/R1 + 1/R2 + 1/R3) =$   
 $\underline{\hspace{2cm}} \Omega$ .

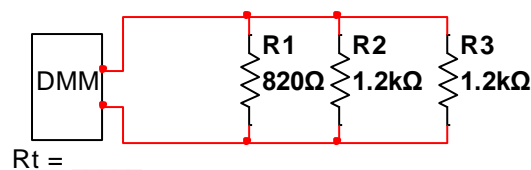
- c) Set up the circuit as shown in Figure 1 using the three resistors, then use the DMM (set to Ohm measurement) to measure the total parallel resistance  $R_t = \underline{\hspace{2cm}} \Omega$ .



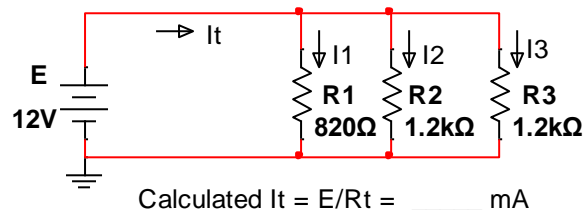
- d) Compare the results obtained from (a) and (b).  
e) Calculate the total circuit current  $I_t = \underline{\hspace{2cm}}$  mA, and record the calculated  $I_t$  in Table 1.



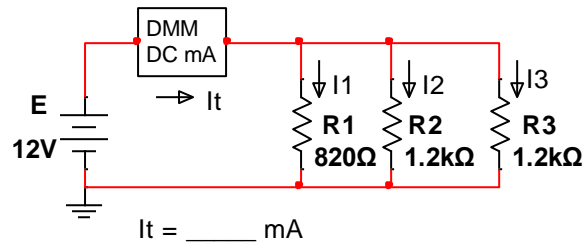
- f) Connect the variable power supply, set to 12V. Use the DMM (set to DC I measurement) to measure the current  $I_t = \underline{\hspace{2cm}}$  mA, and record the  $I_t$  in Table 1.



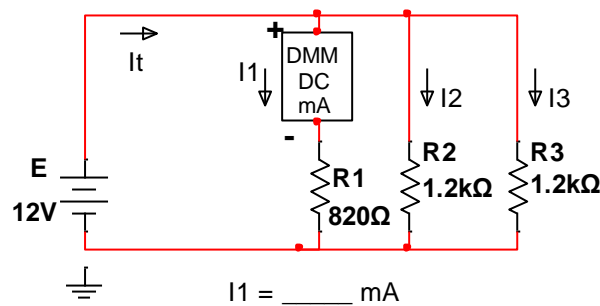- g) Compare the results obtained from (e) and (f).  
 h) Calculate all branch currents  $I_1 = \underline{\hspace{2cm}}$  mA,  $I_2 = \underline{\hspace{2cm}}$  mA, and  $I_3 = \underline{\hspace{2cm}}$  mA and record the values in Table 1.  
 i) Measure the branch circuit currents  $I_1$ ,  $I_2$ , and  $I_3$ , then record their values in the Table 1.
- Connect the DMM as shown below for  $I_1$  measurement



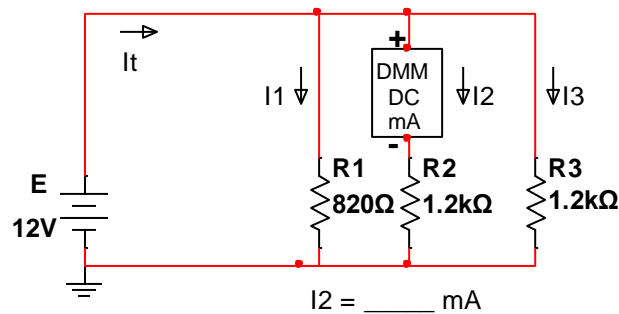- Connect the DMM as shown below for  $I_2$  measurement



- Connect the DMM as shown below for  $I_3$  measurement

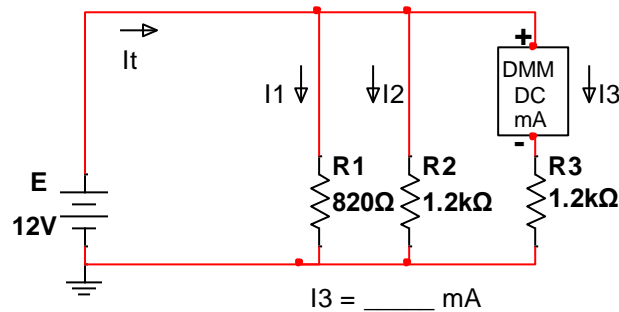



Table 1. Measured and calculated currents

|                   | I1 | I2 | I3 <sub>t</sub> | I <sub>t</sub> |
|-------------------|----|----|-----------------|----------------|
| Calculated values |    |    |                 |                |
| Measured values   |    |    |                 |                |
| Simulated values  |    |    |                 |                |

j) Verifying the KCL

$$I_t = \underline{\hspace{2cm}} = I_1 + I_2 + I_3 = \underline{\hspace{2cm}}$$

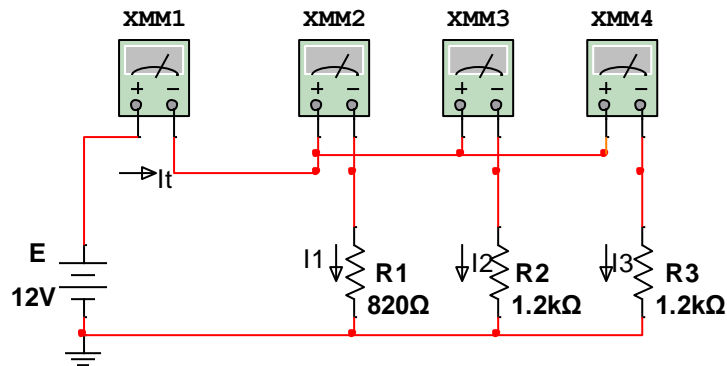Part 2. Prepare a Multisim simulation circuit as shown below. Run the simulated circuit and record I1, I2, I3, and I<sub>t</sub>.



a) Explain among the calculated, measured and simulated values.