

ECET 102/CPET101
Lab 6
Series and Parallel Circuit Lab

By Prof. Paul I. Lin

Required Devices & Equipment:

Resistors: $1.5\text{k}\Omega$ x 1, $1\text{k}\Omega$ x 1, 820Ω x 1, 470Ω x 2
Bread board x 1 with wires, wire strippers and cutters
Variable Power Supply x 1
Digital Multimeter (DMM) x 1

Objectives:

1. Learn to calculate parameters of series and parallel resistor circuits and measurement.
2. Learn to use the Multisim (circuit simulation and design computer tool) for circuit analysis.
3. Learn to construct and measure the series and parallel circuit
4. Learn to compare the three methods of calculation, computer analysis and measurement.

Procedure:

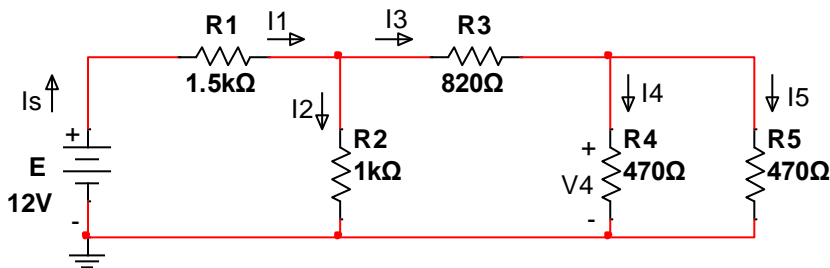


Figure 1. The Series-Parallel Circuit

Part 1. For the circuit shown in Figure 1, calculate R_t , I_s , I_2 , I_4 , I_5 , V_1 , V_2 , V_3 , V_4 and V_5 .

R_t Calculation Procedure

- (a) Remove the power supply, then use the circuit as shown in Figure 2, without power supply to calculate R_t , then record the calculated R_t value in Table 1.

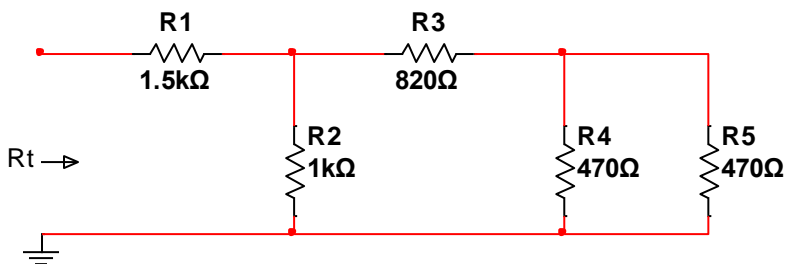


Figure 2. Sub-circuit for R_t calculation

- (b) $R_{45} = R_4 \parallel R_5 = \underline{\hspace{2cm}}$
 (c) $R_{234} = R_3 + R_{45} = \underline{\hspace{2cm}}$
 (d) $R_{2345} = R_2 \parallel R_{234} = \underline{\hspace{2cm}}$
 (e) $R_t = R_1 + R_{2345} = \underline{\hspace{2cm}}$ Ohms

I_s Calculation: $I_s = E/R_t = \underline{\hspace{2cm}}$ mA

V_1 Calculation: $V_1 = I_s * R_1 = I_1 * R_1 = \underline{\hspace{2cm}}$ Volts

V_2 Calculation: $V_2 = E - V_1 = \underline{\hspace{2cm}}$ Volts

I_2 Calculation: $I_2 = V_2/R_2 = \underline{\hspace{2cm}}$ mA

I_3 Calculation (KCL): $I_3 = I_1 - I_2 = \underline{\hspace{2cm}}$ mA

V_3 Calculation: $V_3 = I_3 * R_3 = \underline{\hspace{2cm}}$ Volts

$V_4 = V_5$ Calculation: $V_4 = V_2 - V_3 = \underline{\hspace{2cm}}$ Volts

I_4 Calculation: $I_4 = V_4/R_4 = \underline{\hspace{2cm}}$ mA

I_5 Calculation: $I_5 = I_4 = \underline{\hspace{2cm}}$ mA

Part 2. Computer Analysis using Multisim

- (a) Construct the following circuit for R_t measurement.

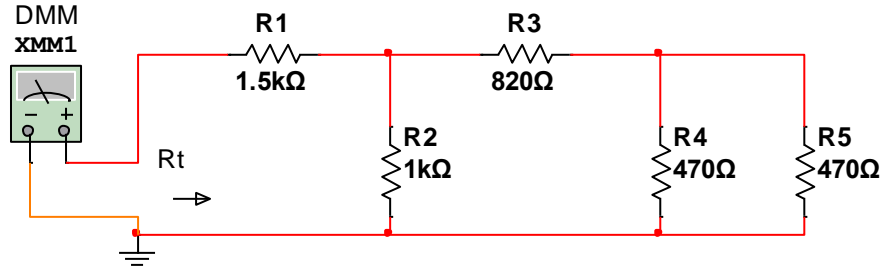


Figure 3. R_t Measurement through Multisim Simulation

- (b) Voltage and Current Measurement

- Add DMM (set to DC mA) for measuring I_s , I_1 , I_2 , I_3 , I_4 , and I_5
- Add DMM (set to DC) for measuring V_2
- Add 4 voltage probes by clicking Place => Probe => Voltage to measure other voltages: V_2 , V_3 , V_4 , and V_5
- Run simulation
- Record all currents and voltages on to Table 1.

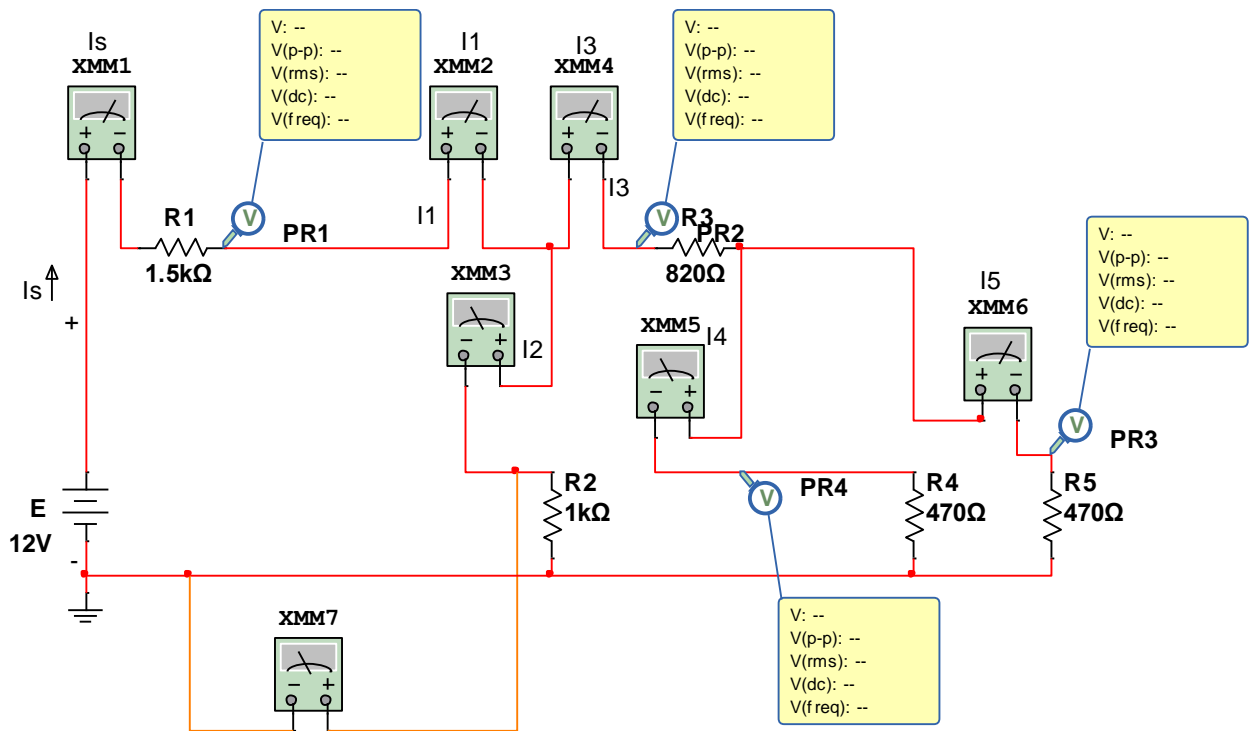


Figure 4. Computer Analysis using Multisim

Part 3. Construct the Circuit as shown in Figure 1 using breadboard.

- (a) Using the DMM, set to DC V measurement, then measure
 voltage across R1 => V1 = _____
 voltage across R2 => V2 = _____
 voltage across R3 => V3 = _____
 voltage across R4 => V4 = _____
 voltage across R5 => V5 = _____

Also record all measured voltage in Table 1.

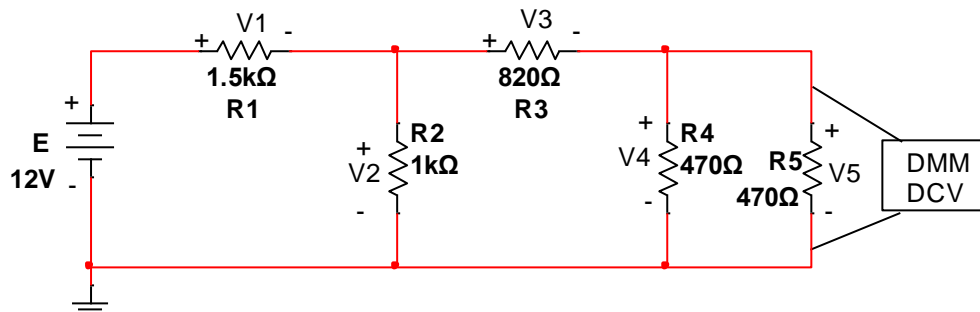


Figure 5. Voltage Measurement using DMM

(b) Current measurement

Use the DMM, set to DC I measurement, then measure and record all currents I_s , I_1 , I_2 , I_3 , I_4 , and I_5 .

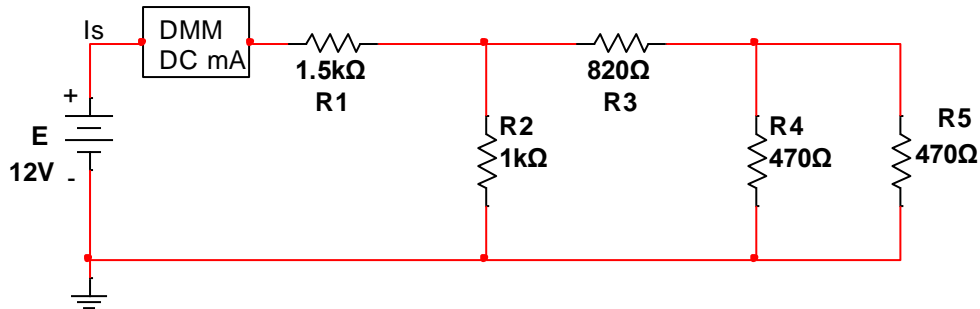


Figure 6. I_s Current Measurement

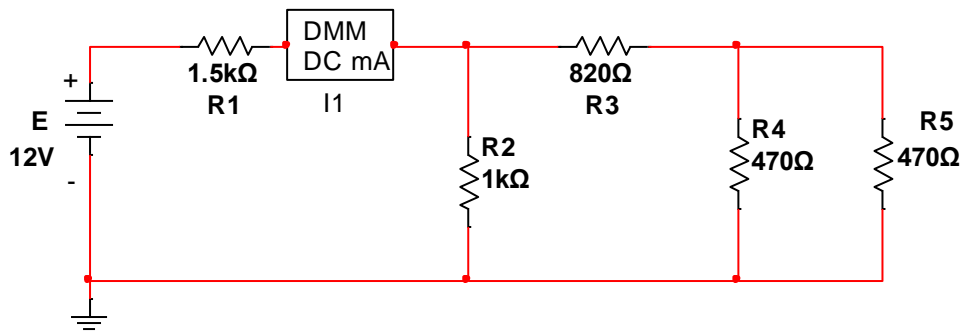


Figure 7. I_1 Current Measurement

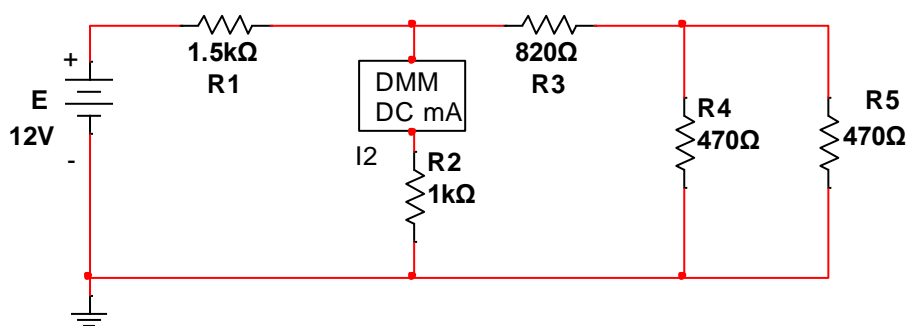


Figure 8. I_2 Current Measurement

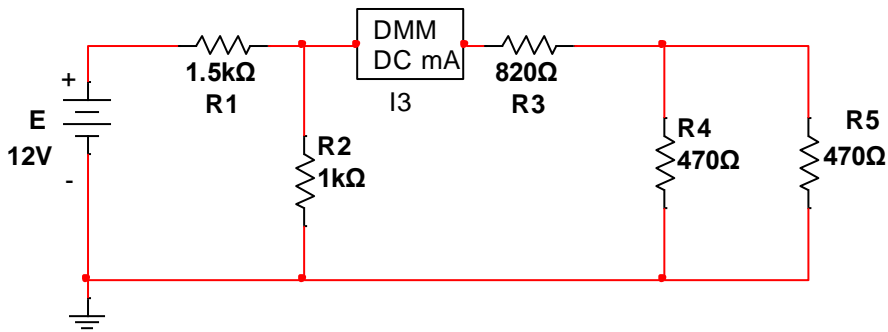


Figure 9. I3 Current Measurement

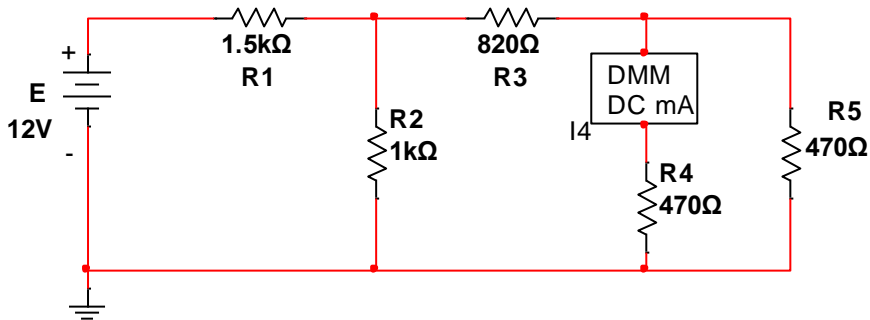


Figure 10. I4 Current Measurement

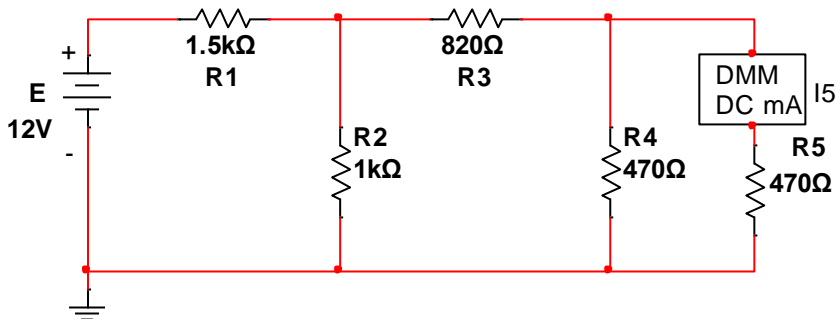


Figure 11. I5 Current Measurement

Table 1. Measured and calculated currents

	Rt	Is	I2	I3	I4	I5
Calculated values						
Measured values						
Simulated values						

	V1	V2	V3	V4	V5
Calculated values					
Measured values					
Simulated values					

Part 4. Compare the three methods of calculation, computer analysis and measurement.