

ECET 102/CPET101
Lab 7
Thevenin's Theorem

By Prof. Paul I. Lin

Required Devices & Equipment:

Resistors: $1\text{k}\Omega \times 2$, $820\Omega \times 1$, $100\Omega \times 1$
Potentiometer $10\text{k}\Omega \times 1$
Bread board $\times 1$ with wires, wire strippers and cutters
Variable Power Supply $\times 1$
Digital Multimeter (DMM) $\times 1$

Objectives:

1. Learn to find a Thevenin equivalent circuit from a more complex circuit using circuit analysis.
2. Using a computer simulation to verify the Thevenin equivalent circuit.

Procedure:

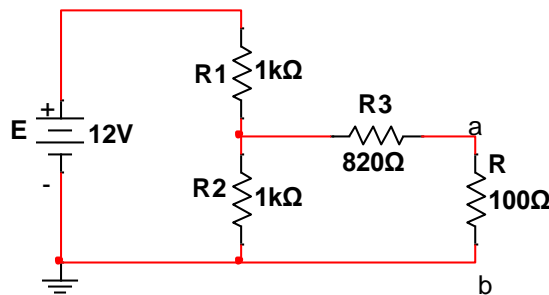


Figure 1. The Circuit for Lab 7

Part 1. Calculation

For the circuit shown in Figure 1, perform the following calculations:

- (a) Find the current through, and the voltage across the resistor, R.
 - 1) Calculate the total circuit resistance $R_T = ((R_3 + R) \parallel R_2) + R_1 = \underline{\hspace{2cm}}$ Ohms.
 - 2) Calculate the total circuit current $I_t = E/R_T = \underline{\hspace{2cm}}$ mA.
 - 3) Calculate the voltage drop across R2, namely $V_2 = E - I_t \cdot R_1 = \underline{\hspace{2cm}}$ Volts.
 - 4) Calculate the current passing through R3 and R, namely $I_r = V_2/(R_3 + R) = \underline{\hspace{2cm}}$ mA.
 - 5) Calculate the voltage drop across R, called $V_{ab} = I_r \cdot R = \underline{\hspace{2cm}}$ Volts
- (b) Find the Thevenin equivalent circuit for the network external to the resistor, R,, namely E_{th} and R_{th} .
 - 1) Remove R from the circuit, as shown in Figure 2, then find open circuit voltage across a and b points called $V_{ab} = E_{th} = E \cdot (R_1 / (R_1 + R_2)) = \underline{\hspace{2cm}}$ Volts.

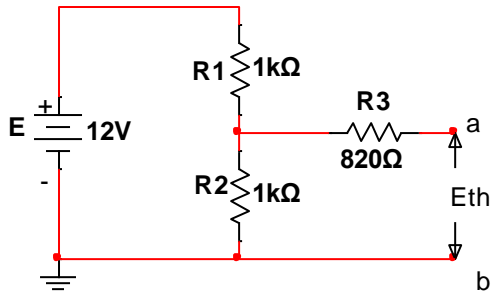


Figure 2. Subcircuit for finding E_{th}

- 2) With E removed, as shown in Figure 3, find the circuit resistance called $R_{th} = (R1 \parallel R2) + R3 = \underline{\hspace{2cm}}$ Ohms.

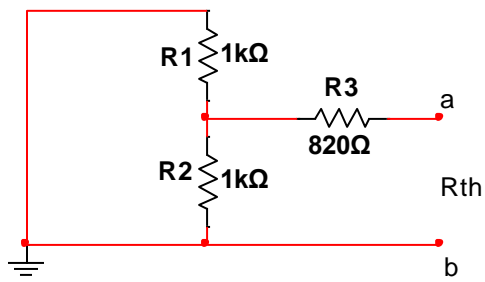


Figure 3. Subcircuit for finding R_{th}

- (c) Using the values calculated for E_{th} and R_{th} , as shown in Figure 4, calculate the current through, and voltage across the resistor, R .

$$I_r = E_{th} / (R_{th} + R) = \underline{\hspace{2cm}} \text{ mA}$$

$$V_{ab} = I_r * R = \underline{\hspace{2cm}} \text{ Volts}$$

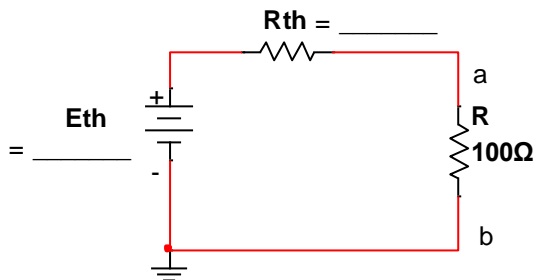


Figure 4. Thevenin equivalent circuit

- (d) Compare the results from (a) and (b)

Part 2. Computer Analysis

- Construct the circuit shown in Figure 4, using Multisim.
- Add an ammeter and a voltmeter to measure the current through R, and voltage across.

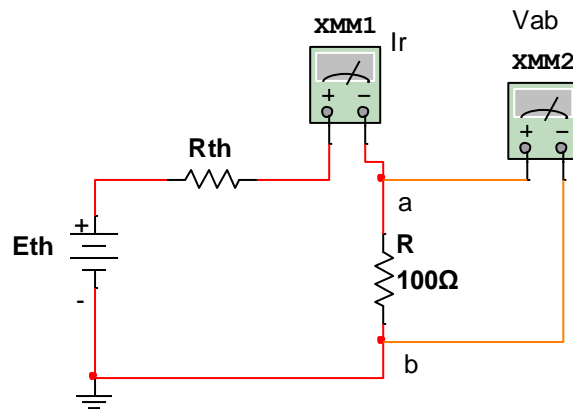


Figure 5. Thevenin equivalent circuit using Multisim Simulation

Part 3. Measurement

- Construct the circuit shown in Figure 1, and measure the current through and the voltage across R.

$I_r = \underline{\hspace{2cm}}$ mA.

$V_{ab} = \underline{\hspace{2cm}}$ Volts

- Using the values of E_{th} and R_{th} calculated in Part 1, duplicate these values with the power supply and a potentiometer.
- Measure the current through and voltage across the resistor R.

$I_r = \underline{\hspace{2cm}}$ mA

$V_{ab} = \underline{\hspace{2cm}}$ Volts

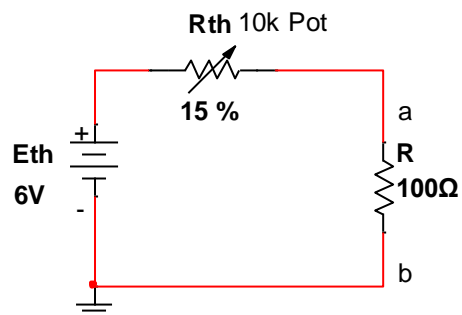


Figure 6. Thevenin equivalent circuit for measurement

Part 4. Compare the three methods of calculation, computer analysis and measurement. Note any differences in the results.