

**ECET 102/CPET101**  
**Lab 8**  
**Maximum Power Transfer Lab**

By Prof. Paul I. Lin

**Required Devices & Equipment:**

Resistors:  $2\text{k}\Omega$  x 2,  $1\text{k}\Omega$  x 1  
Potentiometer  $5\text{k}\Omega$  x 2  
Bread board x 1 with wires, wire strippers and cutters  
Variable Power Supply x 1  
Digital Multimeter (DMM) x 1

**Objectives:**

1. Learn to use the Maximum Power Transfer theorem in circuit analysis.
2. Learn to construct a circuit and measure maximum power transfer to the load.
3. Learn to use a computer simulation to verify the Maximum Power Transfer.

**Introduction:**

The maximum power transfer theorem states that for an electrical circuit with a finite internal source resistance,  $R_s$ , the maximum power transfer from source to the load occurs when the load resistance,  $R_L$ , equals the  $R_s$ , or  $R_L = R_s$ .

Consider the example circuit shown in Figure 1, where  $R_s = 100\Omega$ , and  $R_L$  is a variable resistor between 0 to  $200\Omega$ . The current passing through the circuit is  $I = E/(R_s + R_L)$ , and the power dissipation at the  $R_L$  is  $P = I^2 \cdot R_L$ .

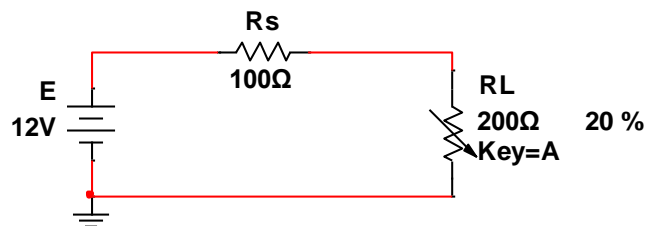


Figure 1. An example circuit

The following Matlab program can be used to calculate the output power, with  $R_L$  changed from 0, 10, 20, ...200 ohms, and compute the corresponding  $I$  and  $P$  for each  $R_L$  step changes. Figure 2 shows the maximum power at  $R_L$  occurs when  $R_L = 100$  ohms.

```
% maxpower.m
Rs = 100;
RL = 0:10:200;
E = 12;
I = E./(Rs + RL);
V_RL = I.*RL;
P = (I.^2).*RL;
subplot(2,1,1),plot(RL, V_RL), grid on, xlabel('RL - Ohms'), ylabel('V_RL - Volt');
subplot(2,1,2), plot(RL, P), grid on, xlabel('RL - Ohms'), ylabel('P - Watts');
```

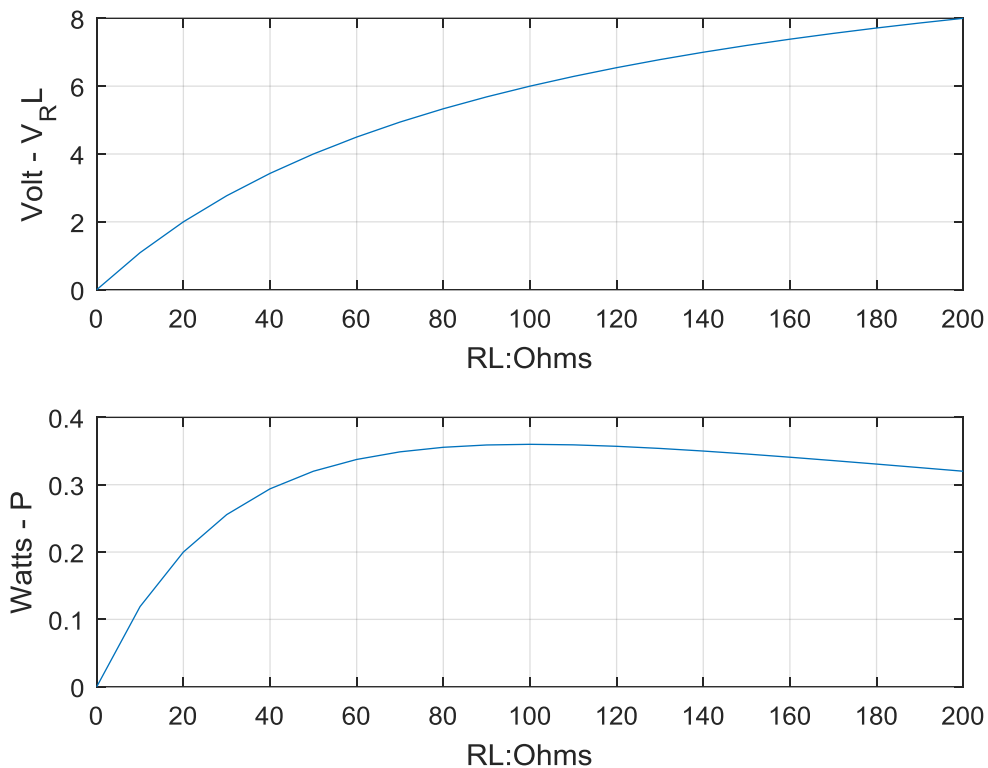


Figure 2. RL vs Vab and RL-P plots

**Procedure:** Consider the circuit shown in Figure 3 for the Lab 8. We will apply the following three methods for maximum power transfer calculation and verification:

- Using Thevenin's equivalent circuit and maximum power transfer circuit transfer theorem to compute the load resistance  $R_L$  for a maximum power transfer.
- Using one of the following computer tools to compute and a plot with the maximum power vs.  $R_L$ :
  - Excel spread sheet, or
  - Matlab program, or
  - Multisim program, configuring a DC Sweep analysis
- Set up a lab circuit to measure the condition for the maximum power transfer.

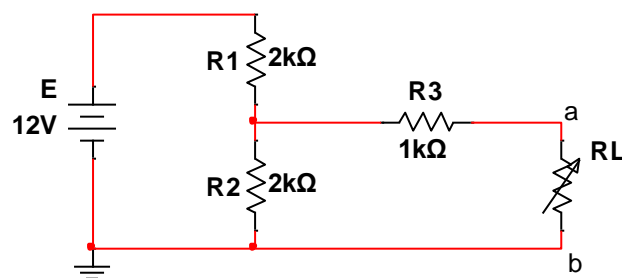


Figure 3. The Circuit for Lab 8

### Part 1. Calculations

For the circuit shown in Figure 3, perform the following calculations:

- (a) Find the Thevenin equivalent circuit related to the load resistor,  $R_L$ , namely  $E_{th}$  and  $R_{th}$ .
- (b) What the value of  $R_L$  should be for a maximum transfer of power.

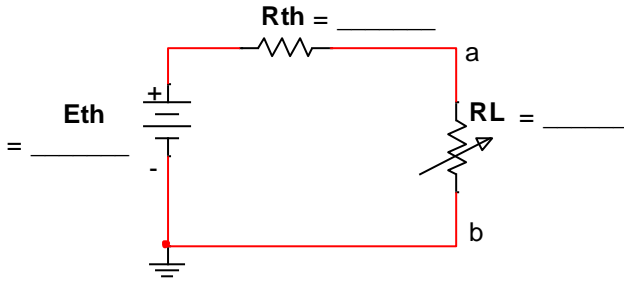


Figure 4. Thevenin equivalent circuit

### Part 2. Measurement

- a) Construct the circuit shown in Figure 5 for measurement.
  - (1) Set the value of  $E_{th}$  as the calculated value from Part1 on the power supply, and measure the current through and the voltage across  $R$ .
  - (2) Set the value of  $R_{th}$  on one of the 5 k $\Omega$  potentiometer.
  - (3) Set the value of  $R_L$  on another 5 k $\Omega$  potentiometer.

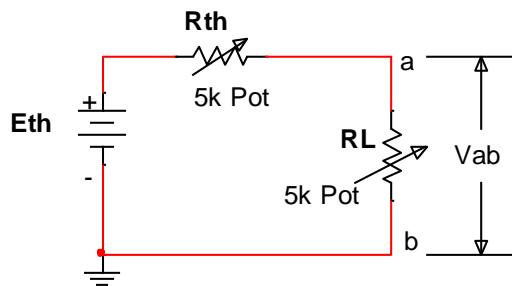


Figure 5. Setup for the measurement

- (4) Vary the value of the  $R_L$  potentiometer above and below the calculated value for maximum power transfer.
- (5) Read and record the voltage across  $R$  for each of the values that are chosen.
- (6) For each value of  $R_L$  used, remove and read the  $R_L$  value with an Ohmmeter.

- (7) Plot the data read, with  $R_L$  values on the X-axis and voltage across  $R_L$  or  $V_{ab}$  on the Y axis.
- (8) What value of " $R_L$ " produces the highest voltage drop across  $R_L$ ?

### **Part 3. Computer Analysis**

- (a) Construct the circuit shown in Figure 5 in a computer program, such as, Multisim.
- (b) Vary the value of  $R_L$  and plot  $R_L$  vs.  $V_{ab}$ , where  $V_{ab}$  is the voltage across the load resistor,  $R_L$ .

**Part 4.** Compare the three methods of calculation, computer analysis and measurement. In particular, compare the  $R_L$  vs.  $V_{ab}$  curves that are obtained with the computer analysis and with the measurement results. Note any differences in the results.