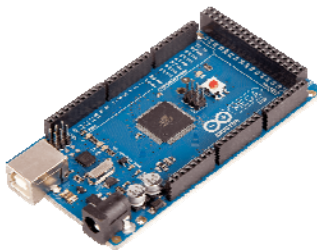


Network-Enabled Sump Pump with Email Alert

Seth Dynes ECET 491

Course Professor

Paul I. Lin, Professor of ECET 491 Senior Design II



1

Table of Contents

- Overview
- Purpose
- Deliverables
- Costs
- Technical
- WBS
- Schedule
- Risk
- Charter

2

Overview

- This system will allow for semi remote monitoring of the sump pit in basements that are prone to flooding.
- Pump failure, heavy rain, a plugged outlet, a power outage or just a rain in the middle of the night all are reasons a basement can flood.
- This system will have audio, visual, and electronic alarms.

3

Purpose

- My system will monitor how much water is in the pits and alert the home owners if they rise above preset levels.
- This would allow the home owner to do other daily tasks around the house without have to constantly check the well pit
- When there is a lot of rain forecasted or there is a risk of popup thunder storms during the night the system will bring home owners peace of mind.


4

Technical

- The operation of the system is very simple. A Sensor measures the water level and the program decides if you should be alerted or not. The sensor uses ultrasound to measure the water level
- Alarms come in three different types: an audio alarm, a visual alarm, and an electronic alarm. The audio alarm will be a bell. The visual alarm will be a flashing light. The electronic alarm is the text or email send to the user.
- Primary power will be from 110 AC Wall power and a secondary power from a 12V DC battery.

7

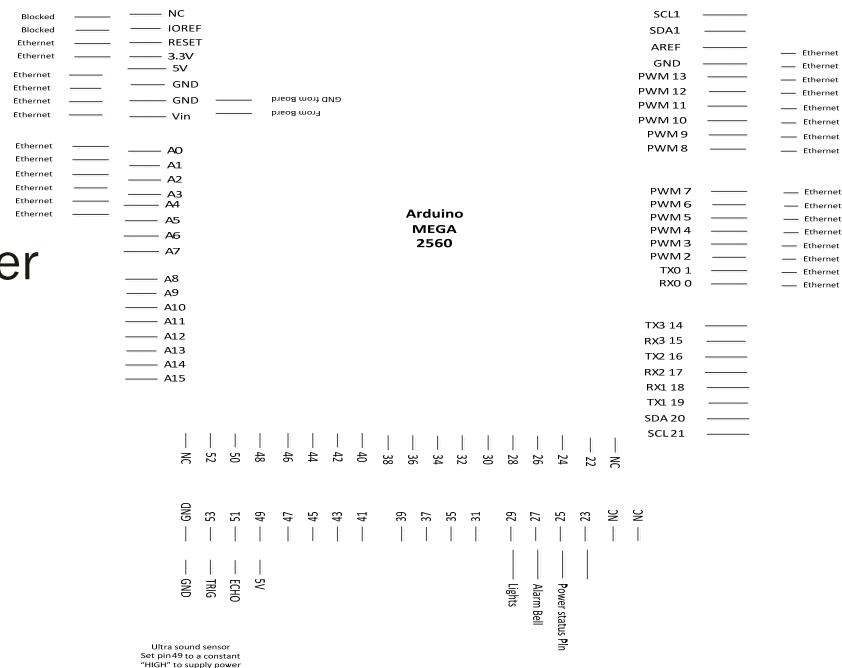Pin Mapping for the Arduino Microcontroller



8

System Requirements

- Shall measure Water in the pit ---**Met**
- Shall have an alarm when the water hits a predetermined level- **Met**
- An alarm shall be audible -**Met**
- An alarm shall be visual -**Met**
- An alarm shall be sent via a network -**Not Met**
- Shall have a backup Battery -**Met**
- Shall maintain a Backup Battery -**Met**

9

Arduino Mega 2560

- It also is the only Arduino Microcontroller that will accept Shields and still have open Input-Output Ports

Microcontroller	ATmega2560
Operating Voltage	5V
Input Voltage (recommended)	7-12V
Input Voltage (limit)	6-20V
Digital I/O Pins	54 (of which 15 provide PWM output)
Analog Input Pins	16
DC Current per I/O Pin	20 mA
DC Current for 3.3V Pin	50 mA
Flash Memory	256 KB of which 8 KB used by bootloader
SRAM	8 KB
EEPROM	4 KB
Clock Speed	16 MHz
LED_BUILTIN	13
Length	101.52 mm
Width	53.3 mm
Weight	37 g

10

One Relay Module:

- It is designed for use with an Arduino Microcontrollers.
- The relay is optimized for low current switching even so provisions are made for the safe current labels.
- This module takes an “Active High” to the signal pin to operate the solenoid.


11

Two Relay module:

- It is designed for use with an Arduino Microcontrollers.
- The relay is optimized for low current switching even so provisions are made for the safe current labels.
- This module takes an “Active Low” to the signal pins to operate the solenoid.

12

Two Relay module:

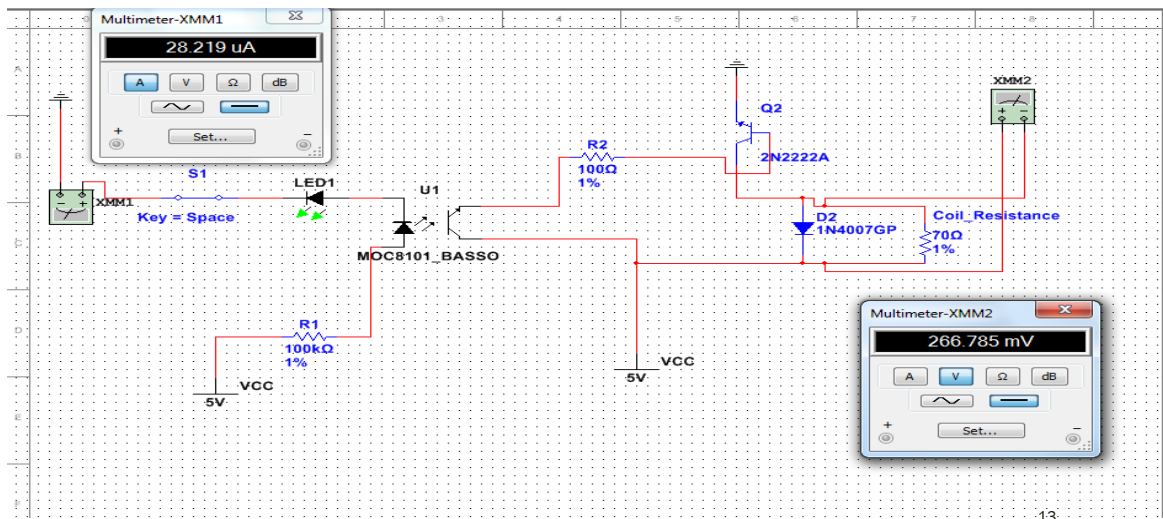

Internet Communication

- **Ethernet Shield:** The expandable board connects the microcontroller to the Internet via a Cat 5E Ethernet cable. The shield has a through hole connectors to allow another shield to be but on top of it. This means that I could stack and operate a WI-FI shield on top yet to offer a choice of Internet connection methods.
- **WI-FI Shield :** The expandable board connects the microcontroller to the Internet via a WA-PA2-Personal protocol.
- The shields are not working right now for technical reasons. (140+ hours spend programming and no luck)

HC-SR04 Ultrasound Sensor:

- This model was chosen because it was designed to be used with the Arduino Microcontrollers and has stock supported code. The code does need to be for a 4 wire sensor.



15

Terminal Strips:

- We are using terminal strips to distribute the power to other parts of the systems. The top strip has +12V and the bottom strip is a common ground. This allows for wiring changes, expansion, and upgrades for any future with ease.



16

Battery:

- A common 12V, 7AH battery is used
- For longer protection a garden tractor battery can be used and instead of the small Sealed-Lead Acid battery that I had on hand.
- For the longer protection times a marine deep cycle 12 DC battery can also be used if extended periods of battery use is expected.

17

Battery Charger:

- An automatic float and trickle charger a supplier will be used to maintain the battery.
- The trickle charger supplies a small amount of current at a voltage level higher than the battery voltage.
- The model used will automatically turn itself on and off as needed to keep the battery in peak condition.


18

LM340TS 7805:

- This is a positive 5 volts voltage regulator that takes between 7 and 20 Volts DC.
- I am using this chip to supply power to the relays.
- I am also sending a signal to the Arduino I/O to tell if the AC power is on.

19

Wiring Diagram

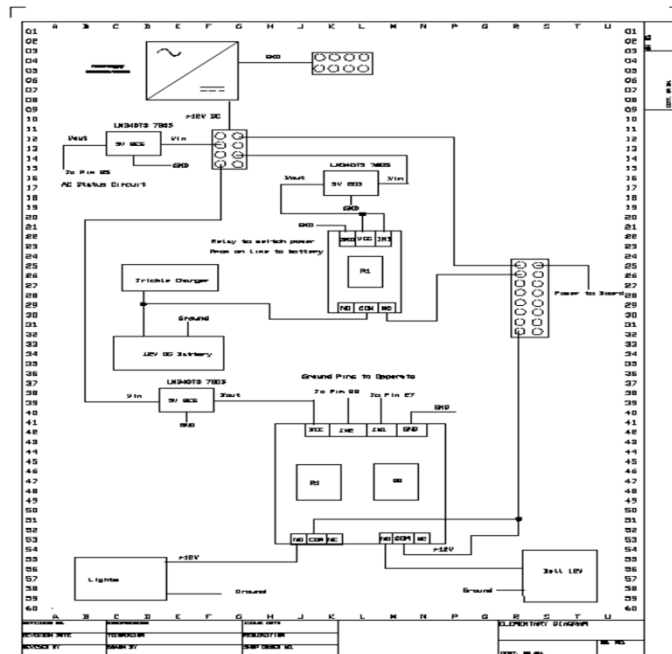

20

Programming States


- Below is the state diagram for the software
- This covers all the major “states” that the program will be in.

Machine States						
Water Level	Status		Has 5 Min Passed?	Water Level	AC Power Bit	Message
Low	Low Water level		Yes	Low	Low	Power Off Pumps Off
Midium	One Pump Running		Yes	Midium	Low	Power Off, 2 Pumps On
High	Both Pumps Running		Yes	High	Low	Power Off, 1 Pumps On
			Yes	Low	High	No Message
			Yes	Midium	High	1 Pump On
Low	AC Power Off		Yes	High	High	2 Pumps On
High	AC Power On		No	xxxxx	xxxx	No Message
						21


Schedule

- On the following slides are the proposed schedule
- In reality programming was tackled first and the mile stones are a more accurate way of measuring progresses
- Over 40 hours spent on the WI-FI Shield
- Over 140 hours spent of the Ethernet Shield

Schedule

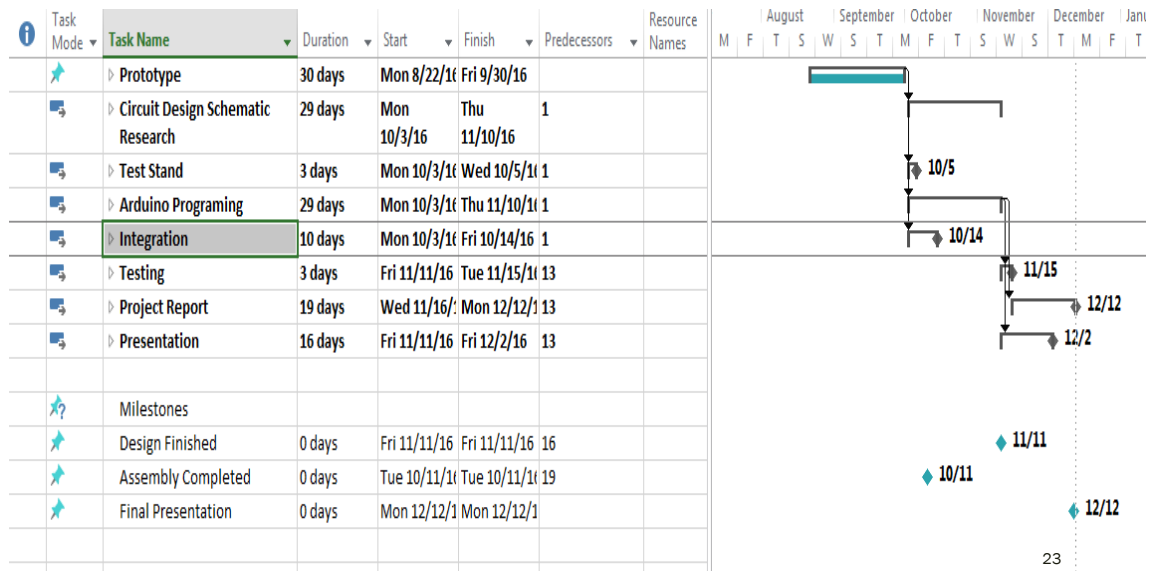

Schedule

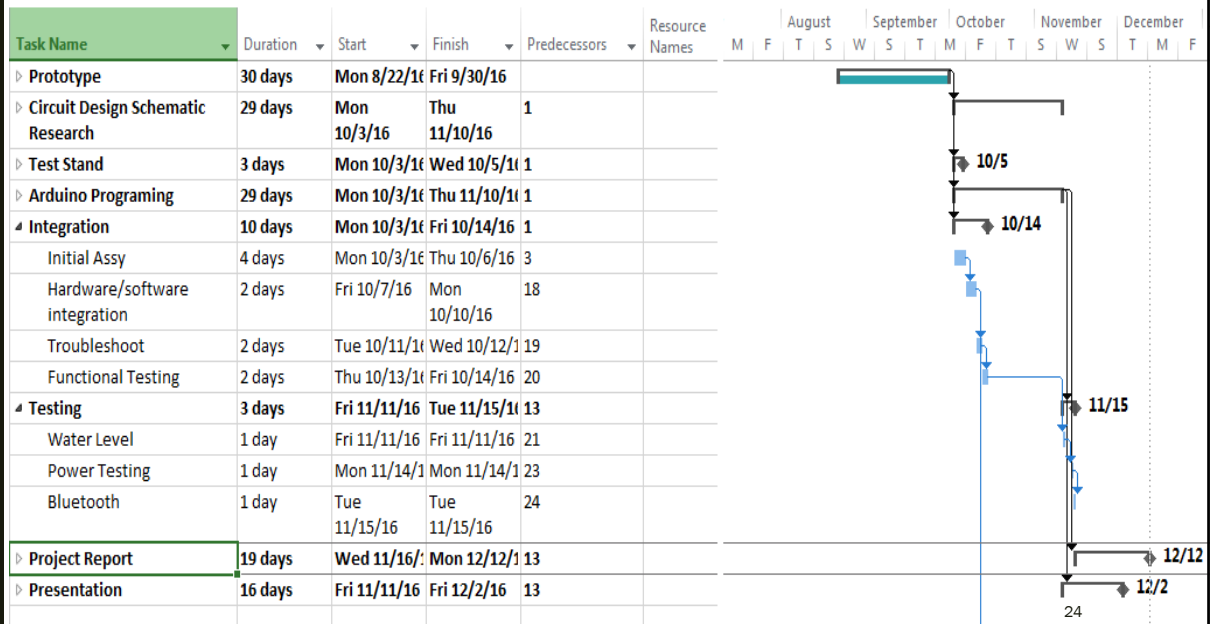

Lessons Learned

- An email is easier to send than a text message so early on in the programming the decision was made to send an email instead.
- The Wi-Fi shield that I was planning on using would not work with the WAPA-2 Enterprise protocol so I made the decision to find an Ethernet shield and code the program with this in mind.
- This would have affected the final presentation on the project as they like to have a working circuit when you give the presentation.

25

Lessons Learned

- Using predesigned components can save time in the design processes,
- For a final production piece a printed circuit board with surface mounted components is the way to go.
- This is very much a prototype design to prove proof of concept and to evaluate under long term testing variables that cannot be measured or predicted in a lab environment.
- For example real word testing of the sensor with the sump pit to find how much interference moving water has on the readings, and ways to increase accuracy.

26

Lessons Learned

- Obsolete components are hard to troubleshoot (Wi-Fi 101 new board)
- Connecting to the Internet is tricky
- Surface mount parts do go bad on Printed Circuit Boards
- Possibly burned the Ethernet Shield
- SMS Shield for texting is a possible work around

27

Conclusion

- The circuit was build with off the shelf components to create a working prototype that will allow the design team to prove the concepts and allow for real world testing to be carried out.
- Future versions of the design can include Wi-Fi101, Bluetooth, Applications for smart phones, and user defined push buttons and status lights that are labeled.
- I believe many homeowners and small business owners would benefit from the peace of mind that the device would bring.

28

Demonstration

29

Questions?

30

Work Cited

- <https://www.arduino.cc/>
- <http://www.talonix.com/shop/category.aspx?catid=281>